

# Lecture 13: CMOS Amplifiers: The Differential Pair - Third Part


**Javier Ardila**

**Reference: Razavi (Fundamentals) - Chapter 10**


Integrated Systems Research Group – OnChip

Universidad Industrial de Santander, Bucaramanga - Colombia

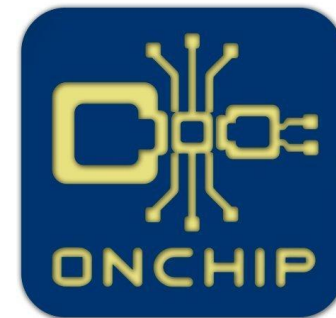[javier.ardila@e3t.uis.edu.co](mailto:javier.ardila@e3t.uis.edu.co)




# Effect of Finite Tail Impedance

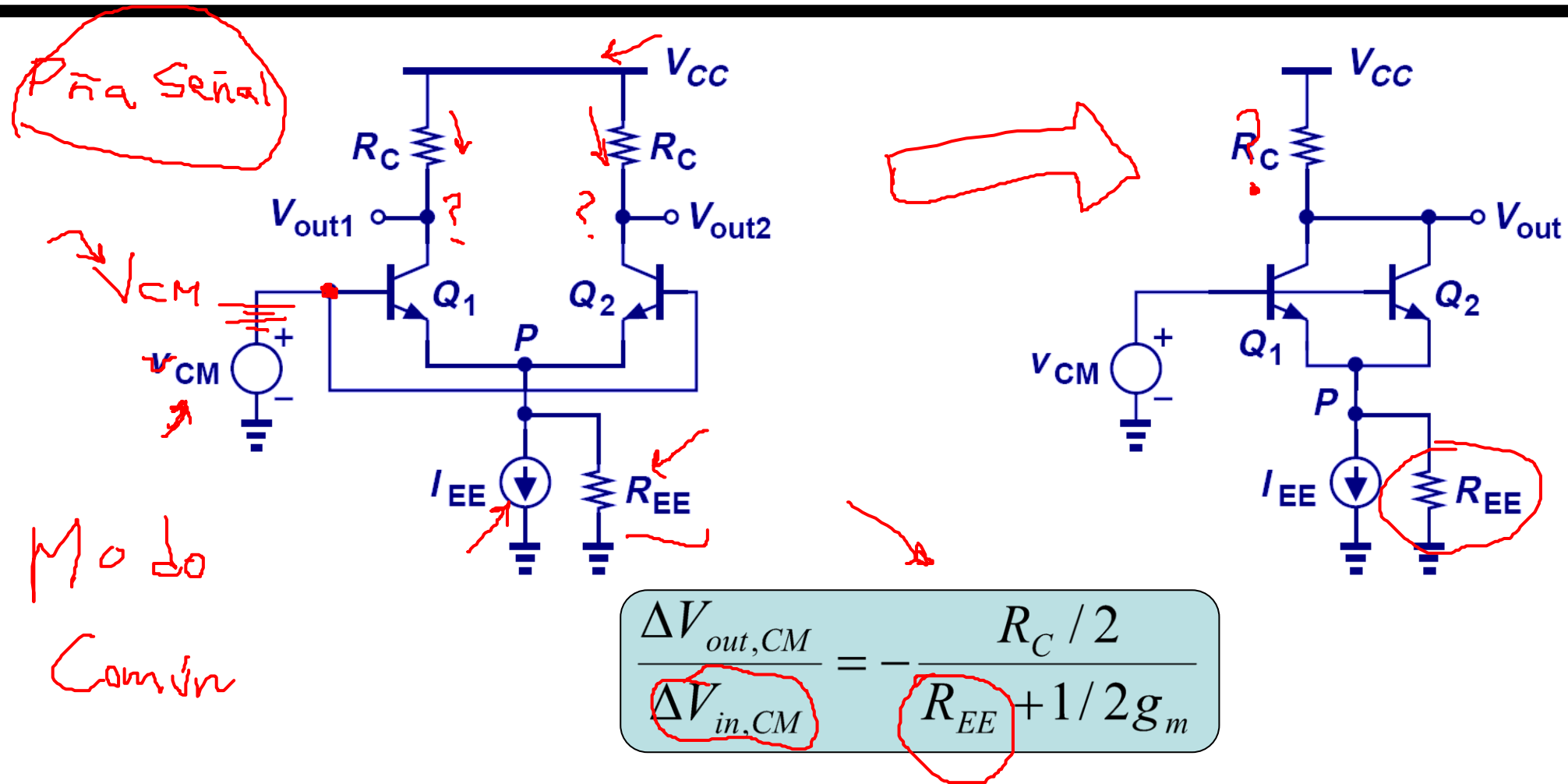


- If the tail current source is not ideal, then when an input CM voltage is applied, the currents in Q<sub>1</sub> and Q<sub>2</sub> and hence output CM voltage will change.


# Input CM Noise with Ideal Tail Current

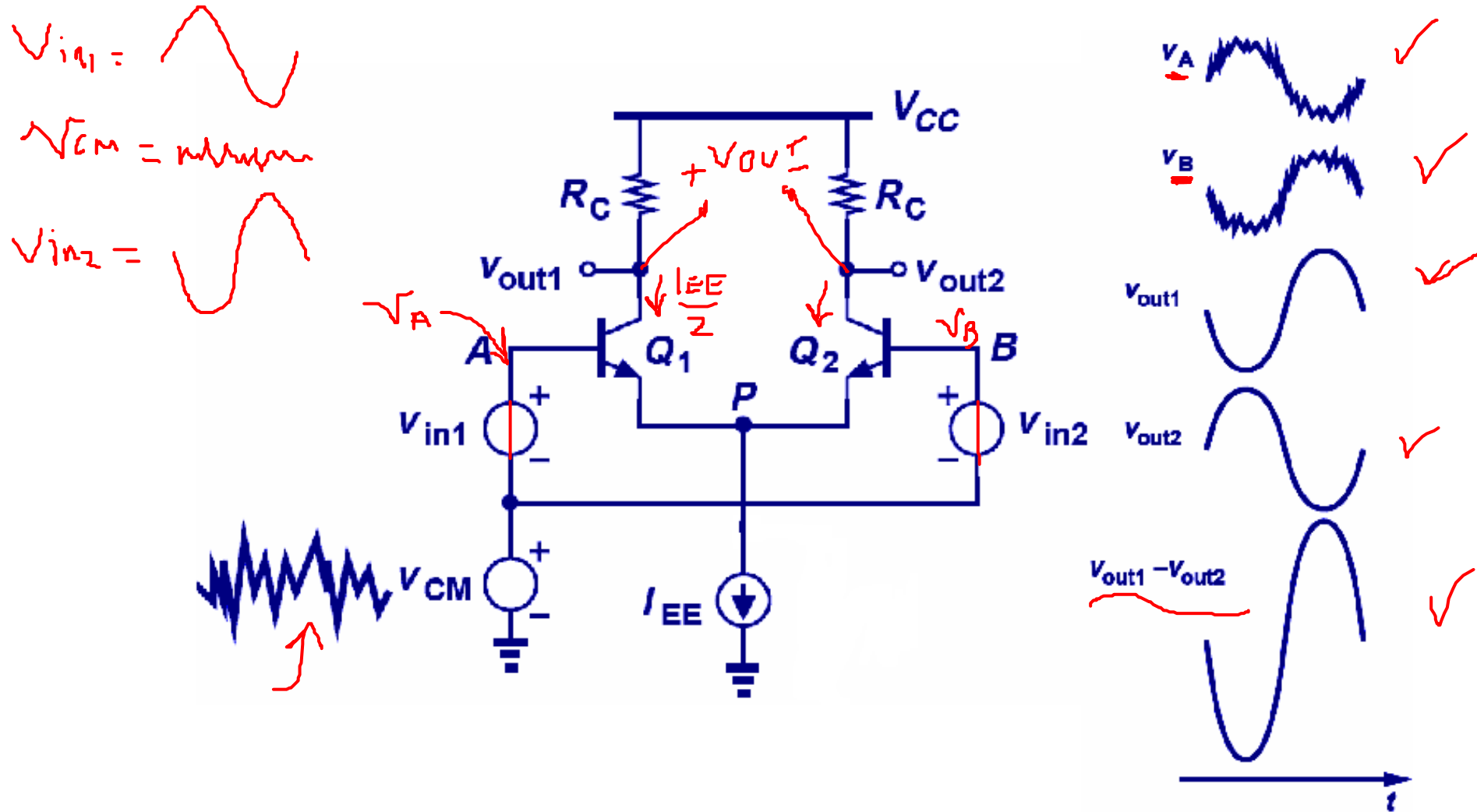
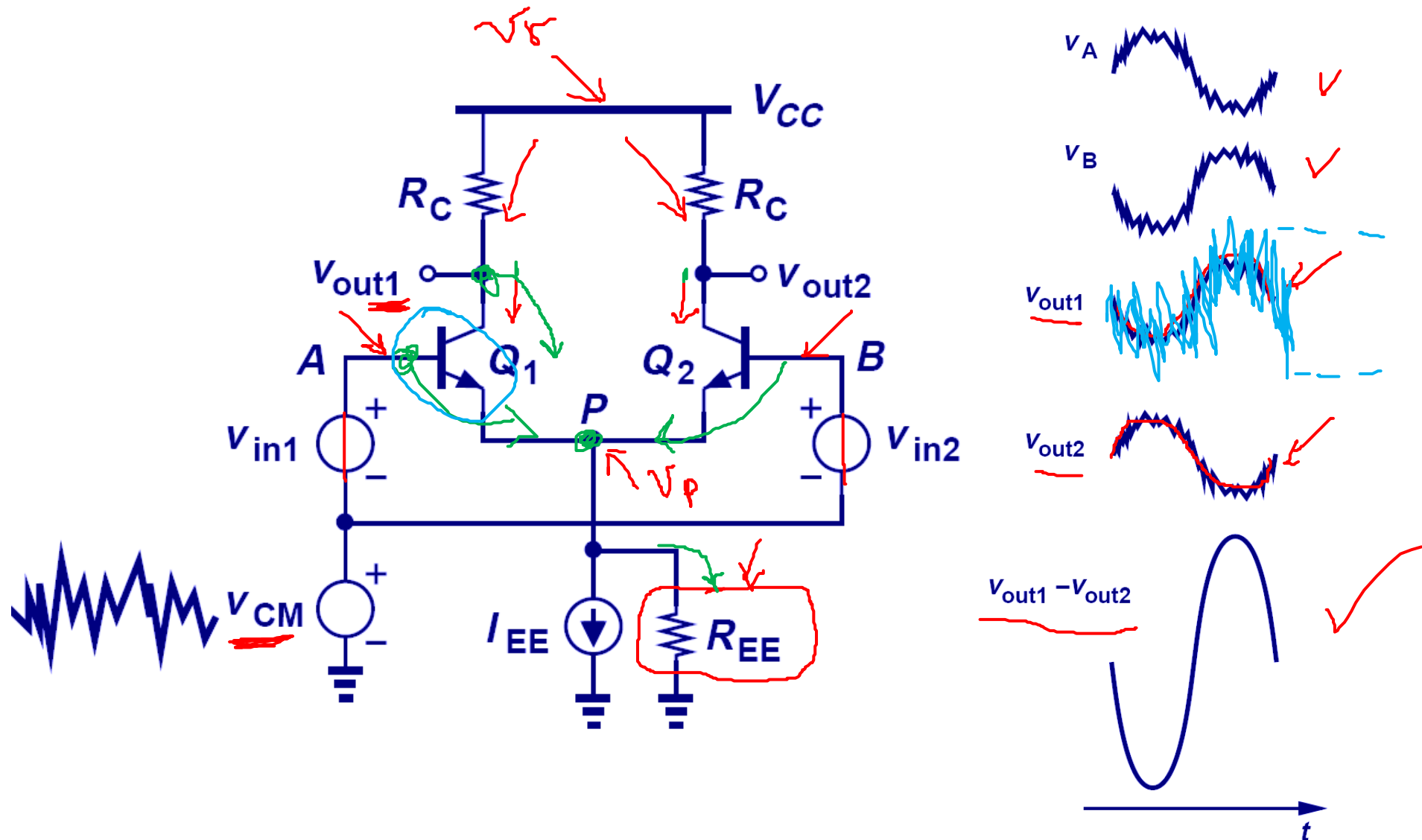
# Input CM Noise with Non-ideal Tail Current



# Comparison - Tail Current

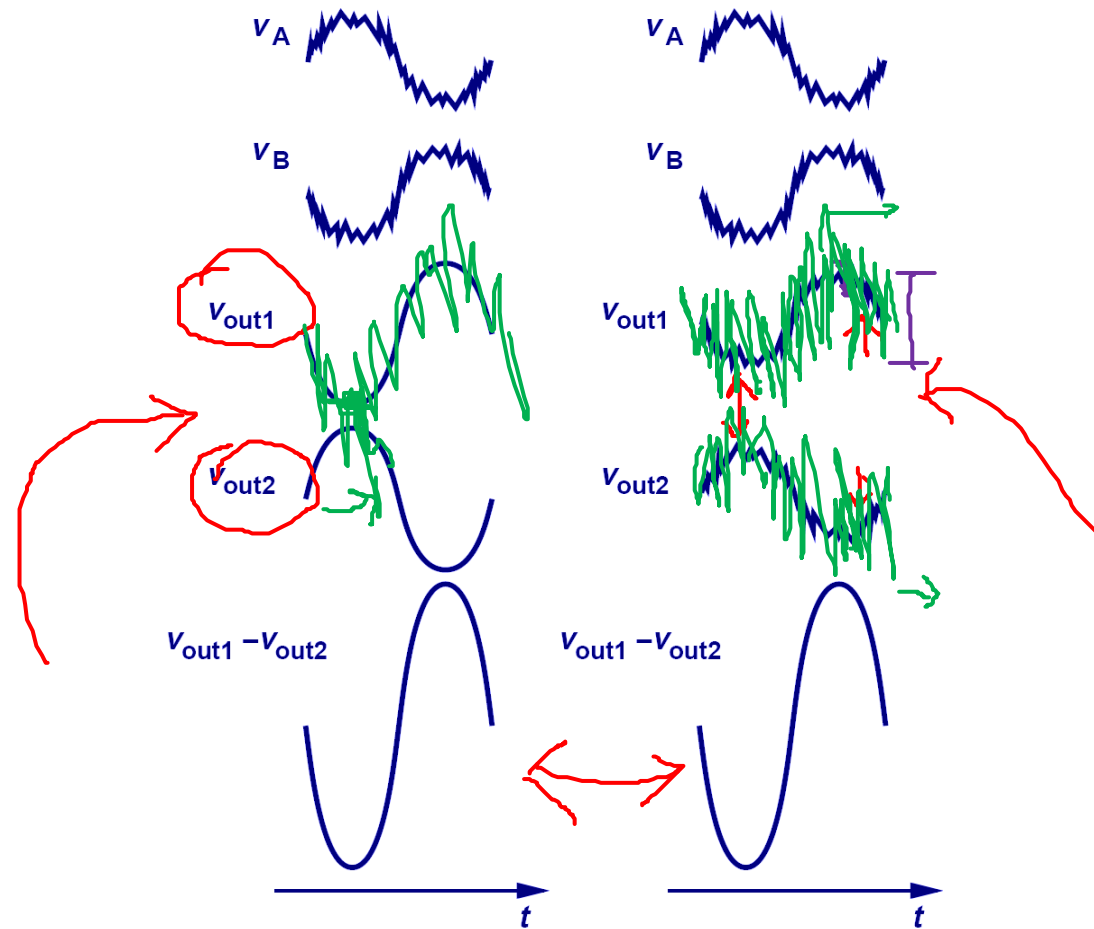

- As it can be seen, the differential output voltages for both cases are the same. So for small input CM noise, the differential pair is not affected.


# Comparison - Tail Current

---

## Common Mode Explanation



.

# CM to DM Conversion, $A_{CM-DM}$

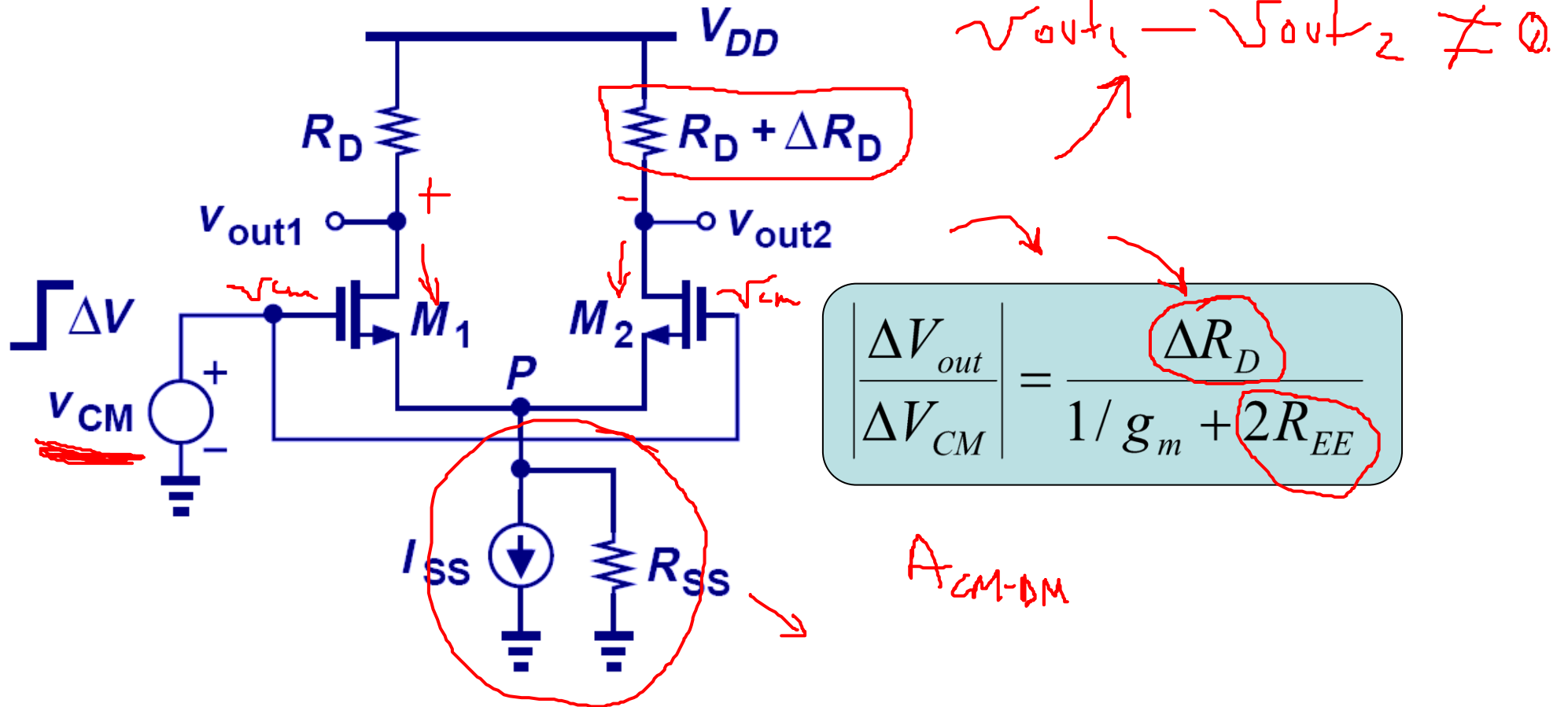

- If finite tail impedance and asymmetry are both present, then the differential output signal will contain a portion of input common-mode signal.


# Example: $A_{CM-DM}$

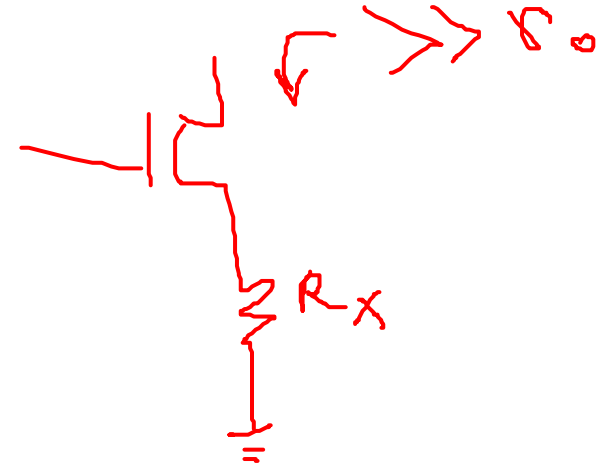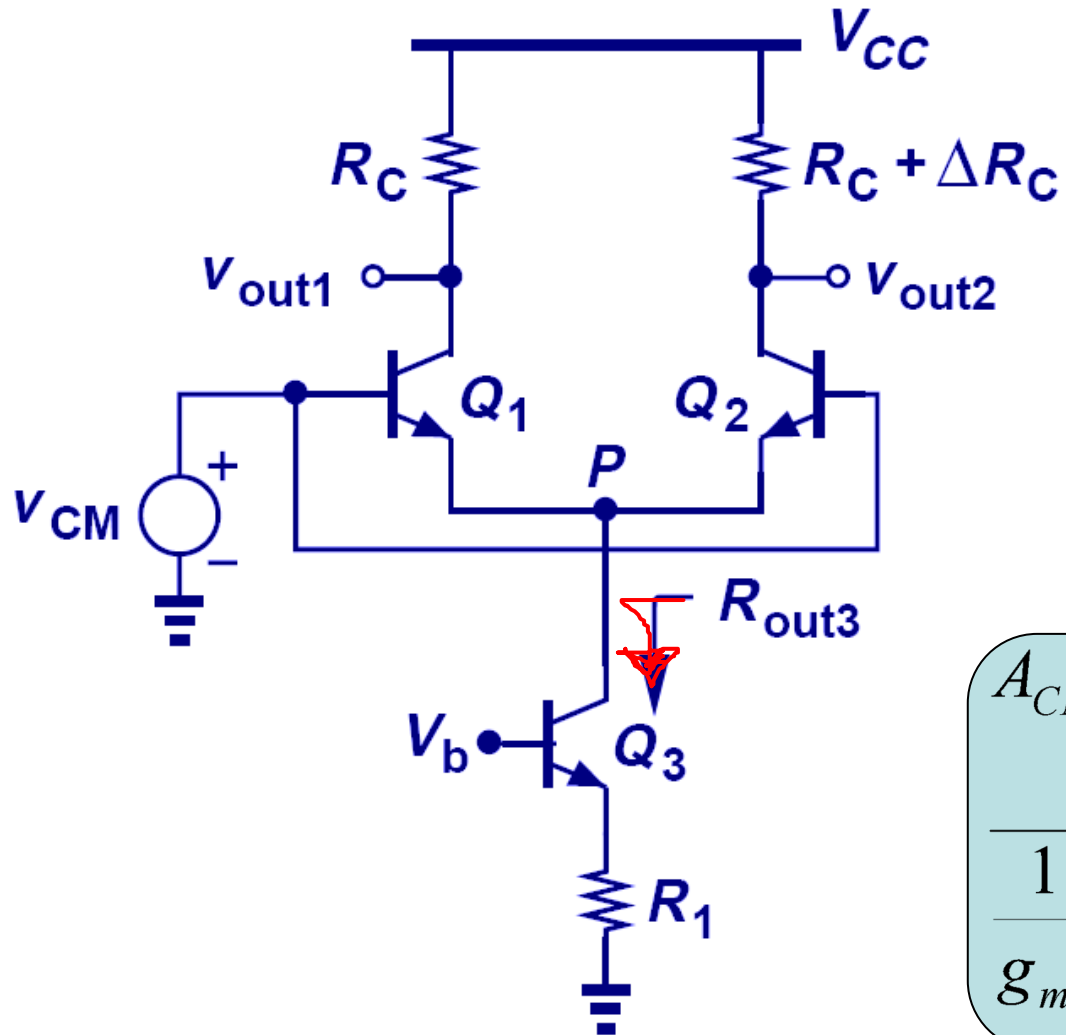

$$A_{CM-DM} = \frac{\Delta R_C}{\frac{1}{g_{m1}} + 2[[1 + g_{m3}(R_1 \parallel r_{\pi 3})]r_{O3} + R_1 \parallel r_{\pi 3}]}$$



# CMRR

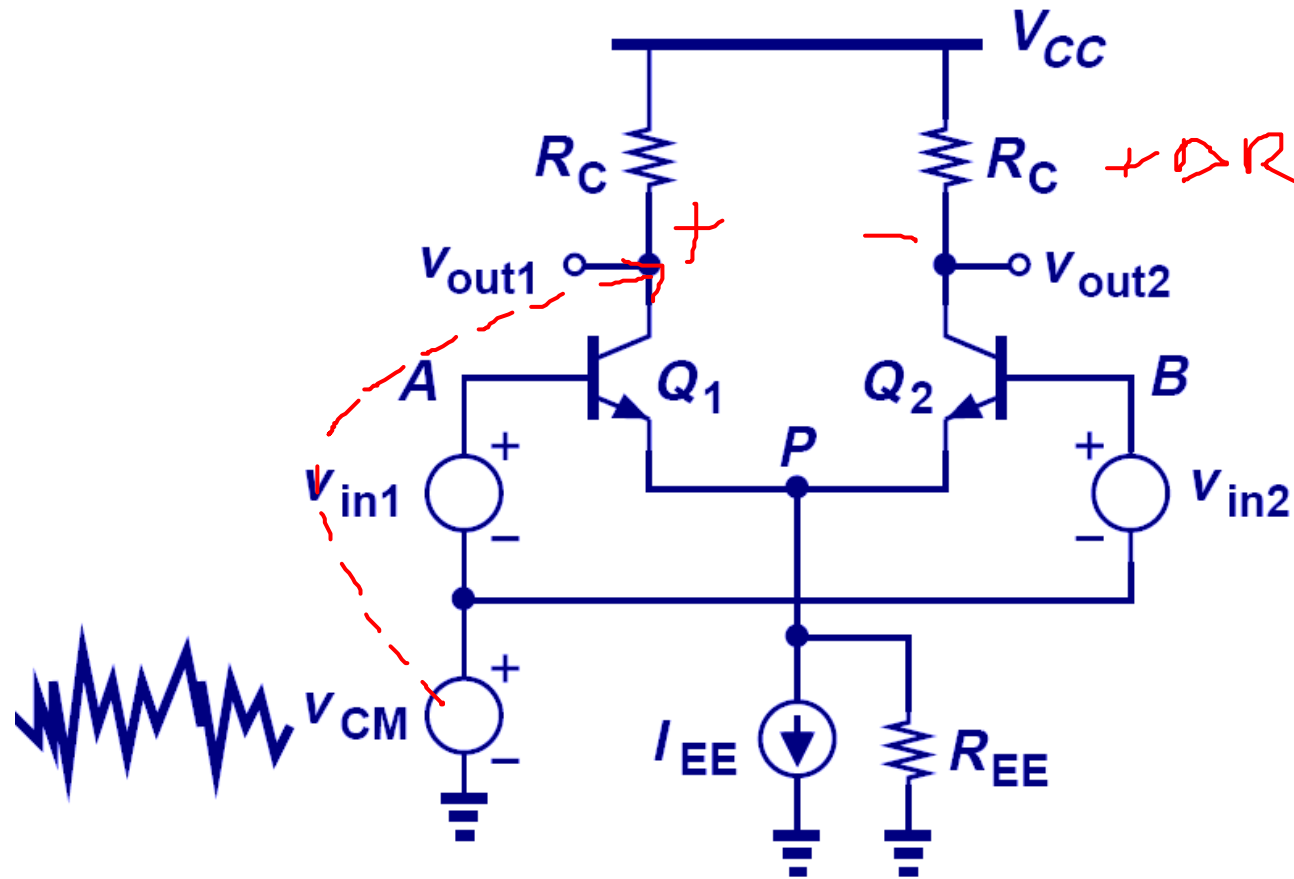


$$CMRR = \frac{A_{DM}}{A_{CM-DM}}$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$


- CMRR defines the ratio of wanted amplified differential input signal to unwanted converted input common-mode noise that appears at the output.
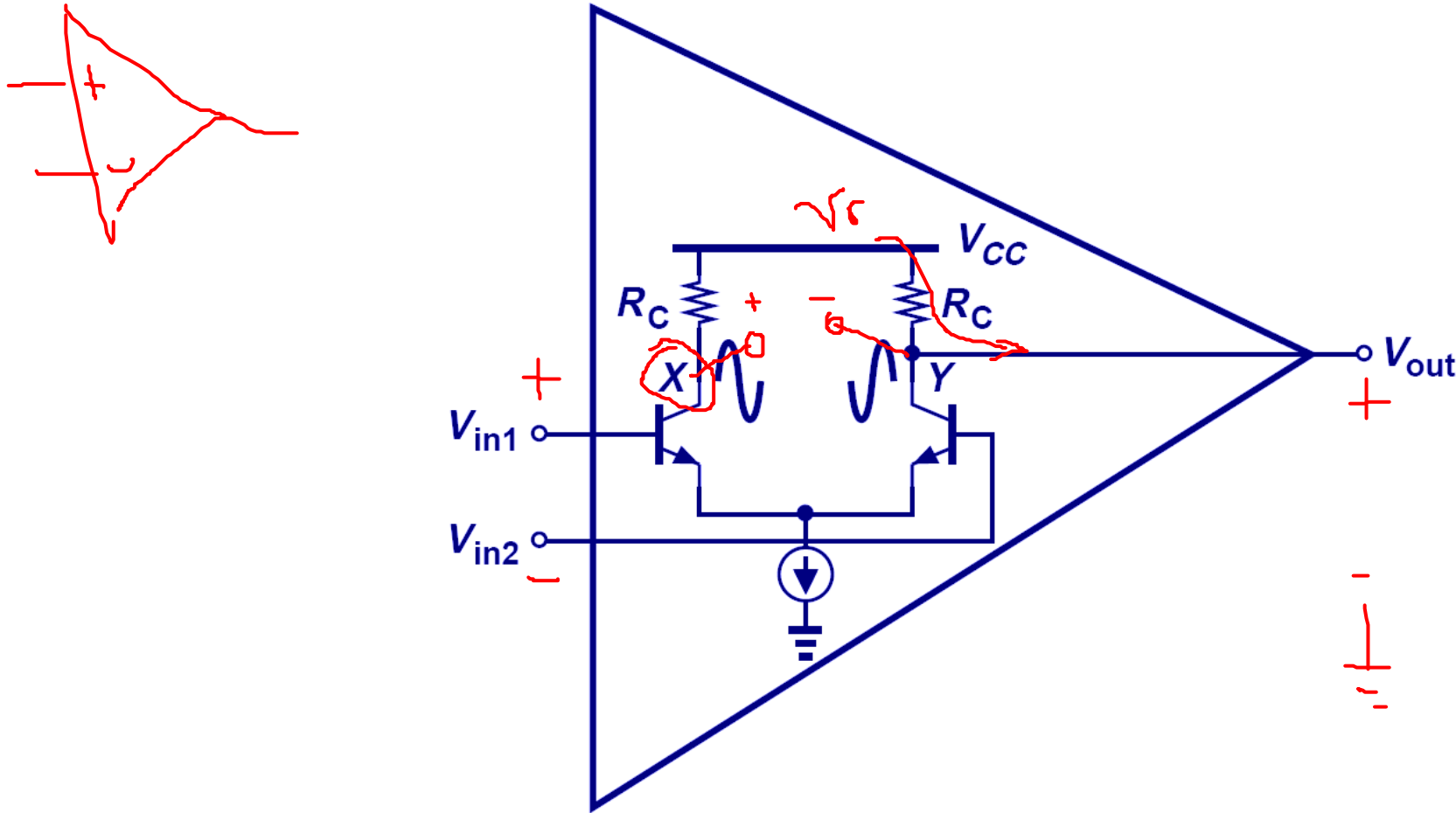
# Differential to Single-Ended Conversion




- Many circuits require a differential to single-ended conversion, however, the above topology is not so good.

# Supply Noise Corruption

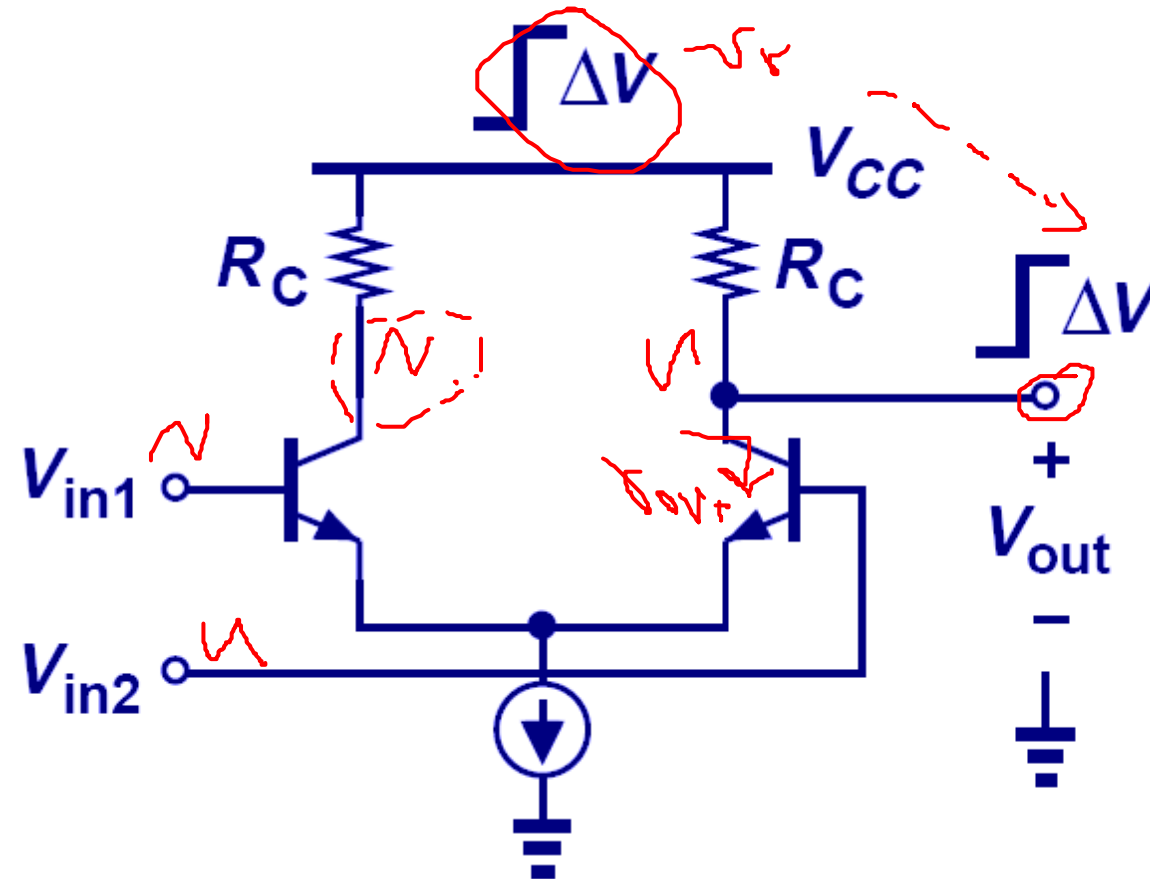



- The most critical drawback of this topology is supply noise corruption, since no common-mode cancellation mechanism exists. Also, we lose half the signal.

# MOS Differential Pair with Active Load

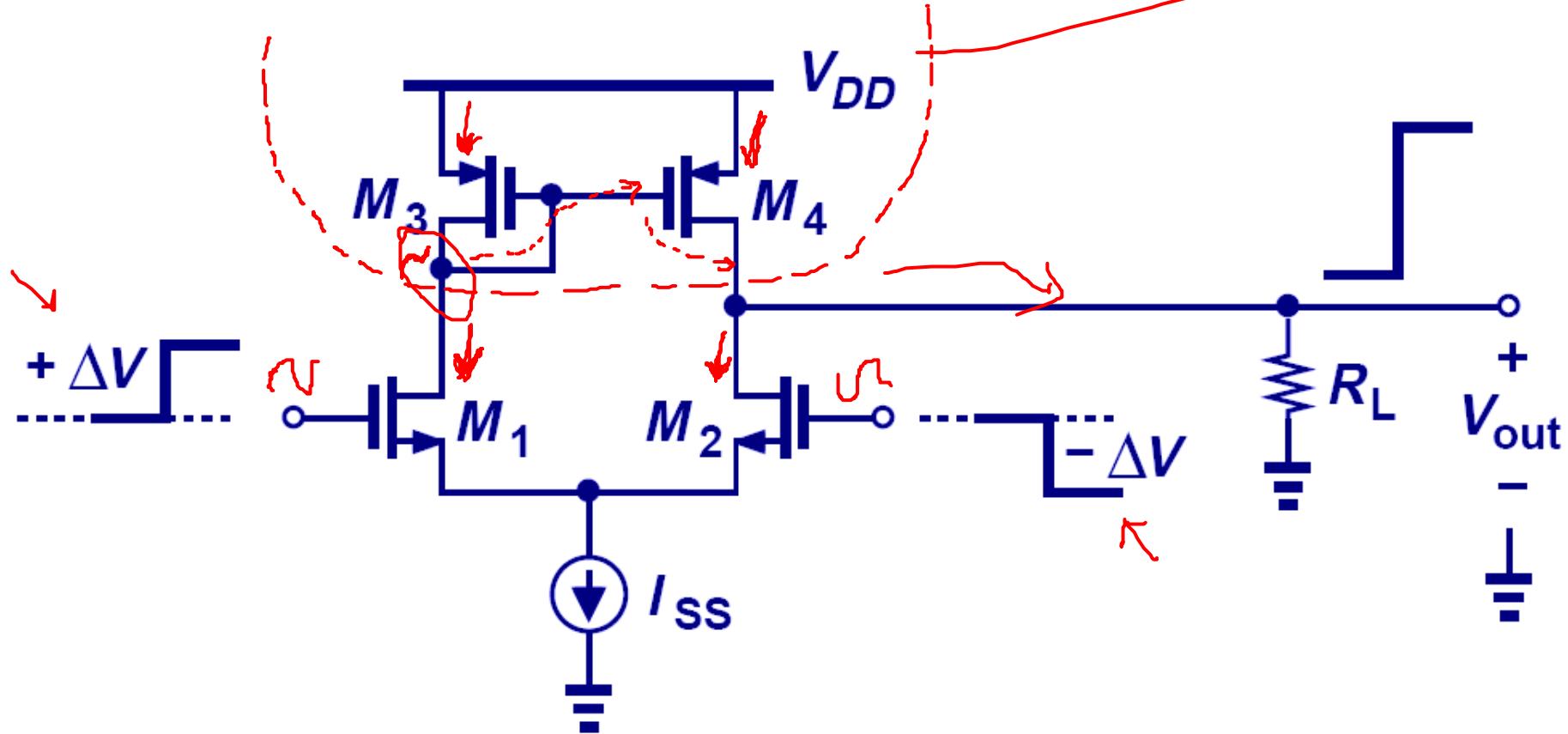


- Similar to its bipolar counterpart, MOS differential pair can also use active load to enhance its single-ended output.

# Active Load vs. Static Load

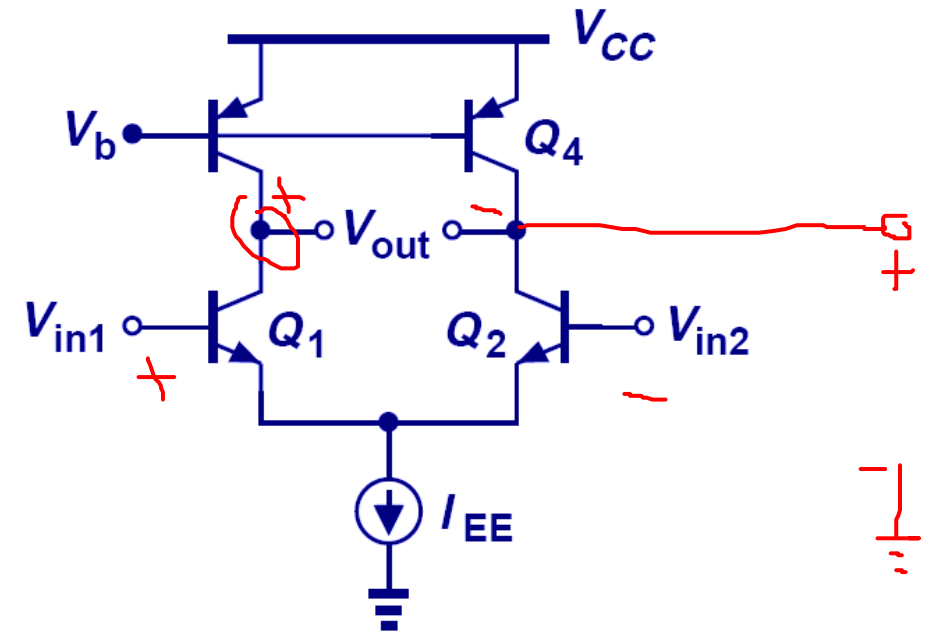
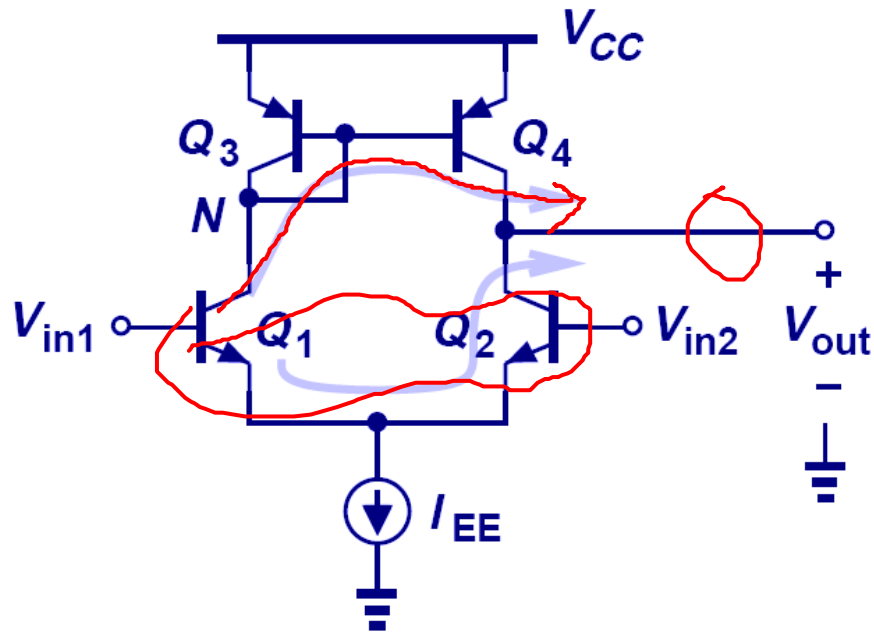


- The load on the left responds to the input signal and enhances the single-ended output, whereas the load on the right does not.

# Asymmetric Differential Pair

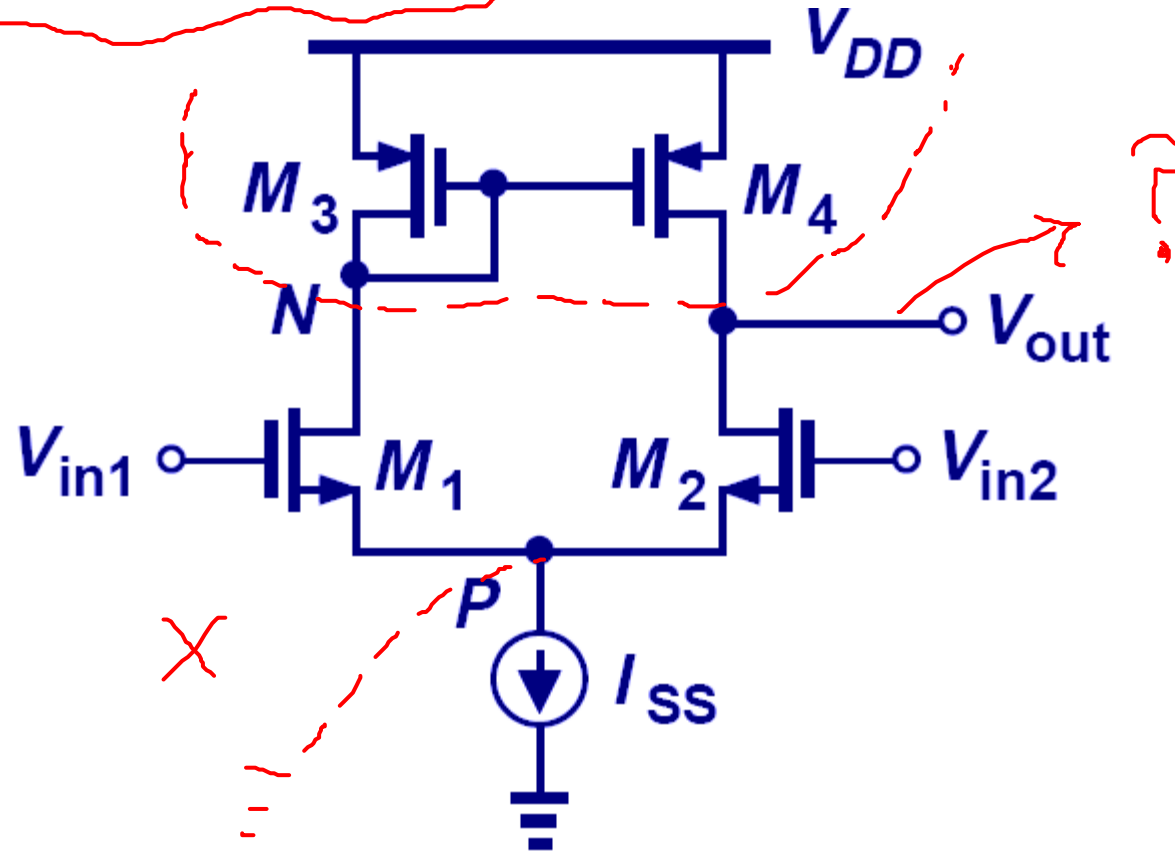

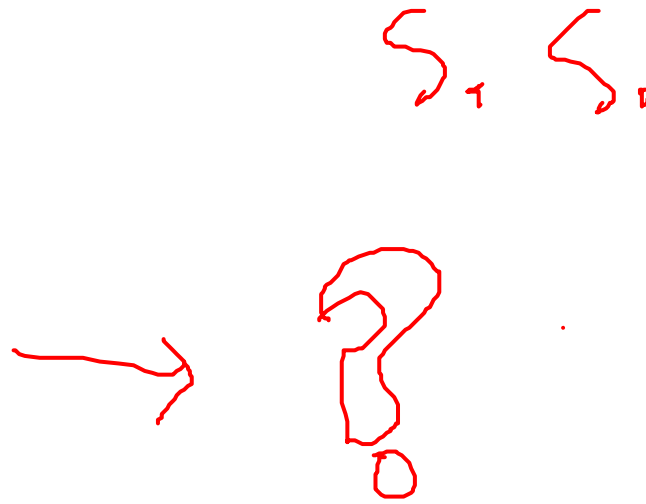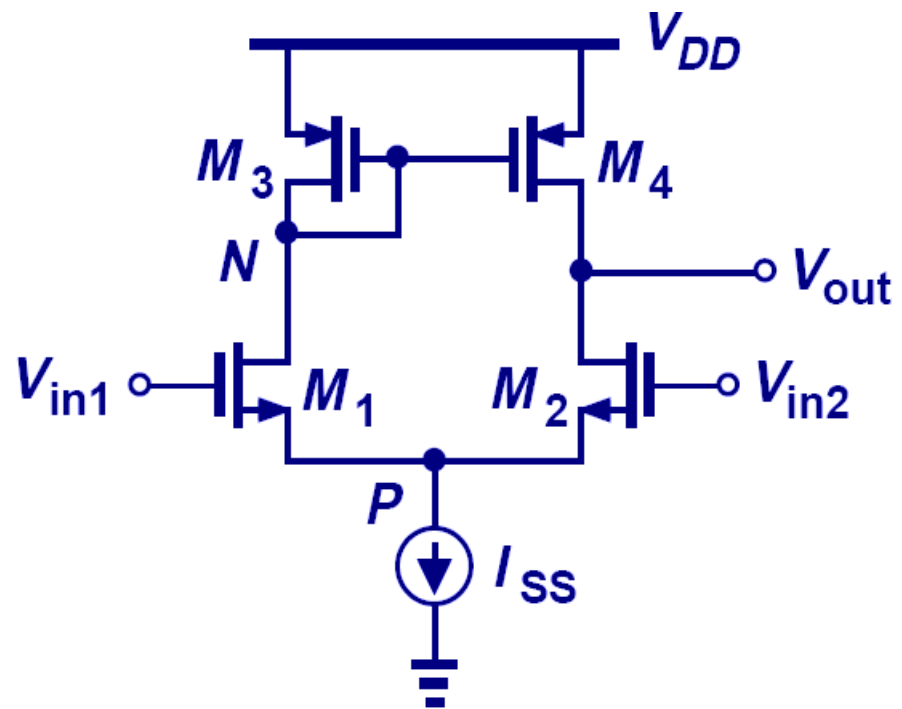- Because of the vastly different resistance magnitude at the drains of  $M_1$  and  $M_2$ , the voltage swings at these two nodes are different and therefore node  $P$  cannot be viewed as a virtual ground.













# Thevenin Equivalent of the Input Pair

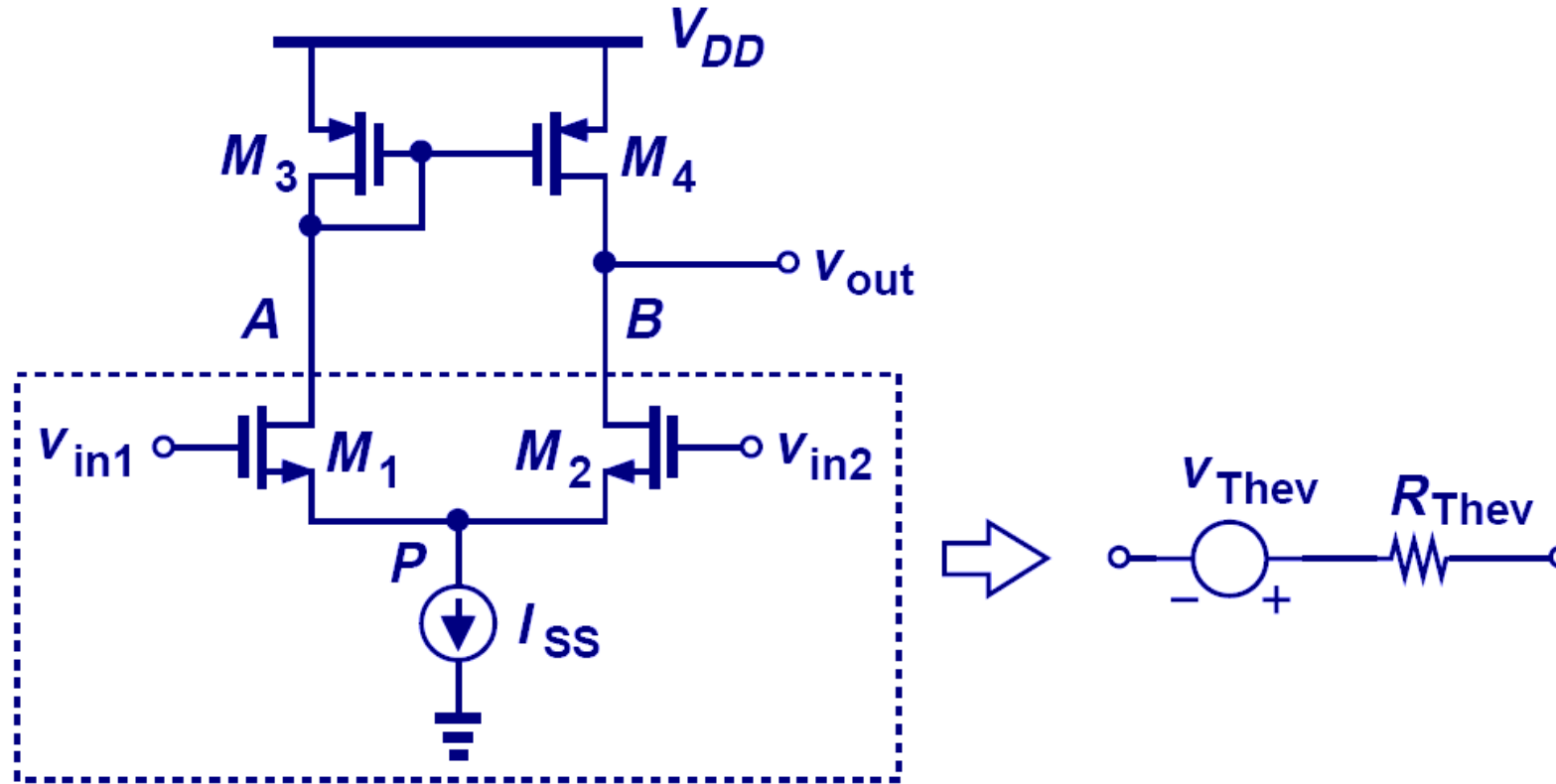

$$v_{Thev} = -g_{mN} r_{oN} (v_{in1} - v_{in2})$$


$$R_{Thev} = 2r_{oN}$$
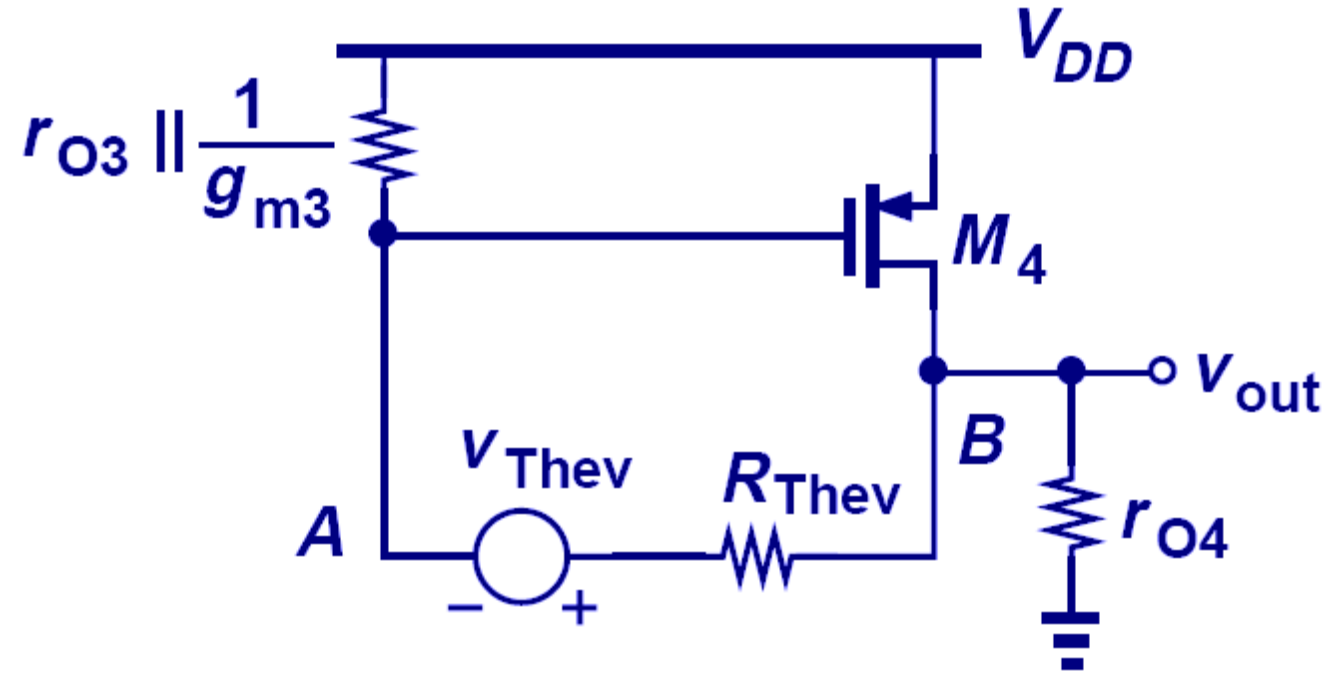
# Simplified Differential Pair with Active Load



$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN} (r_{ON} \parallel r_{OP})$$

# Proof of $V_A \ll V_{out}$


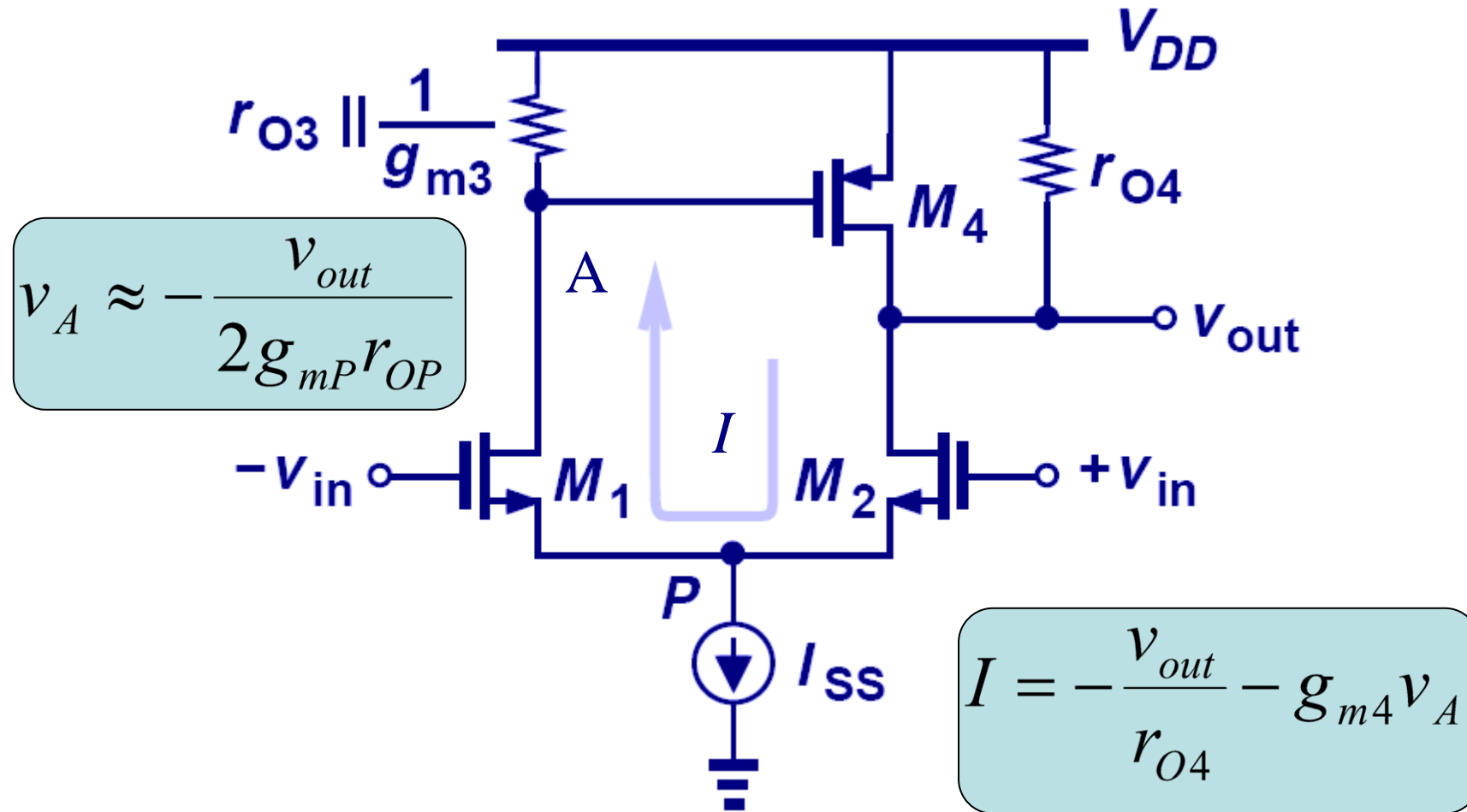

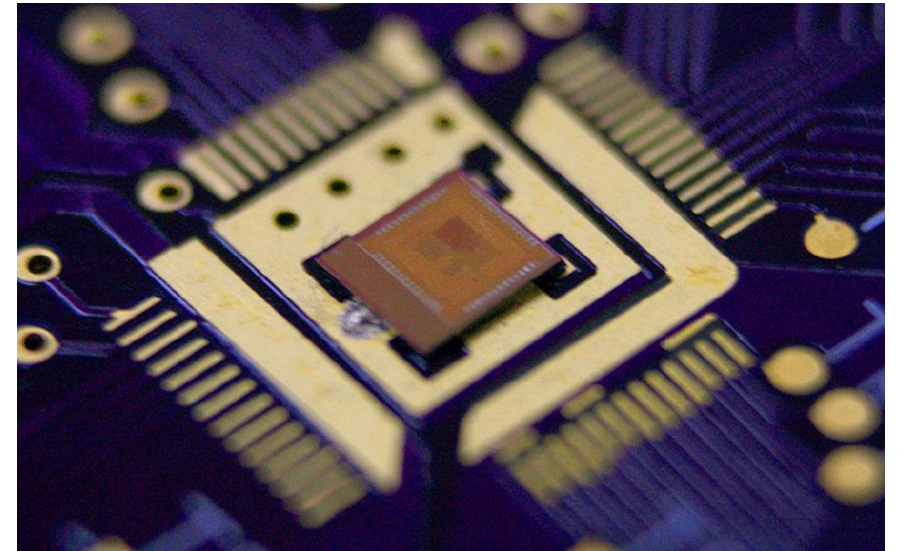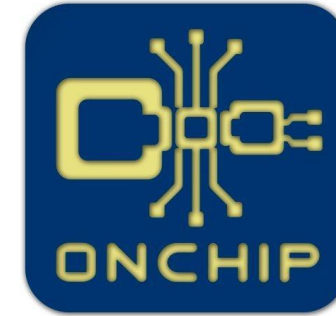
# Thanks

---



*[javier.ardila@correo.uis.edu.co](mailto:javier.ardila@correo.uis.edu.co)*



**@onchipUIS**