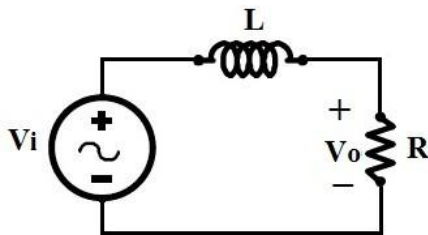


PASIVE FILTERS OF FIRST AND SECOND ORDER WITH RLC ELEMENTS

Diego Jimenez Alvernia, IEEE Student Member and Jesús Torres
 School of Electrical, Electronics and Telecommunications Engineering
 Universidad Industrial de Santander
 diegojalvernia@gmail.com

I. LOW-PASS FILTER

A. RL CIRCUIT



- Transfer function

$$H(s) = \frac{\frac{R}{L}}{s + \frac{R}{L}}$$

- Cut-off frequency

$$\omega_c = \frac{R}{L}$$

- Maximum Amplitude if $j\omega = 0$

$$|H(j\omega)|_{max} = 1$$


- Angle

$$\theta(j\omega) = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{R}{L}}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

B. RC CIRCUIT

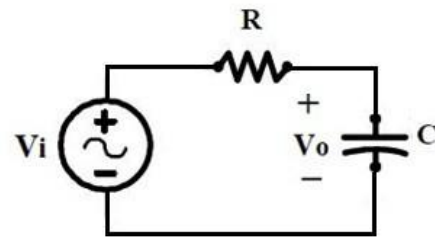

- Transfer function.

$$H(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

- Cut-off frequency

$$\omega_c = \frac{1}{RC}$$

- Maximum Amplitude if $j\omega=0$


$$|H(j\omega)|_{max} = 1$$

- Angle

$$\theta(j\omega) = -\tan^{-1}(\omega RC)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{1}{RC}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

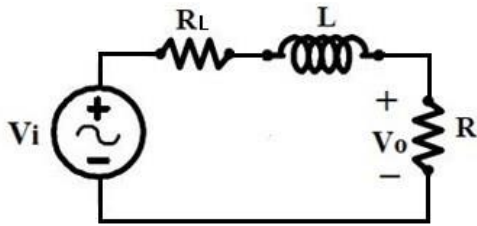C.RL CIRCUIT AND R_{load} SERIES


- Transfer function
-

$$H(s) = \frac{\left(\frac{R_L}{R + R_L}\right)}{s + \left(\frac{R}{L}\right)}$$

- Cut-off frequency

$$\omega_c = \frac{R_e}{L}$$

Where


$$R_e = \frac{R * R_L}{R + R_L}$$

- Maximum Amplitude if $j\omega = 0$

$$|H(j\omega)|_{max} = 1$$

if $j\omega = \infty$

$$H(j\omega) = 0$$

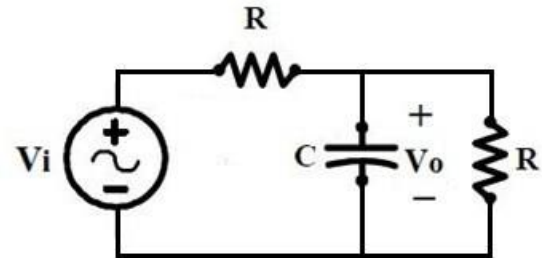 E. RC CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{\frac{R}{L}}{s + \frac{R + R_L}{L}}$$

- Cut-off frequency

$$\omega_c = \frac{R_e}{L}$$

- Maximum Amplitude if $j\omega=0$


$$|H(j\omega)|_{max} = \frac{R}{R + R_L}$$

If $j\omega = \infty$

$$H(j\omega) = 0$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{R}{L}}{\sqrt{\omega^2 + \left(\frac{R + R_L}{L}\right)^2}}$$

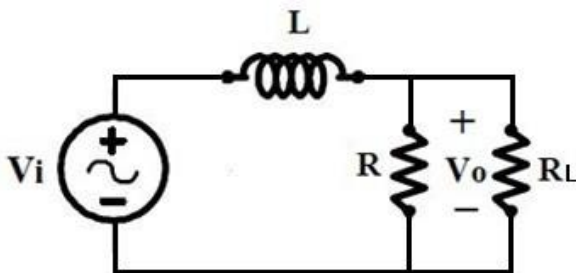 D. RL CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{\frac{1}{RC}}{s + \left(\frac{1}{RC}\right)\left(\frac{R + R_C}{R_C}\right)}$$

- Cut-off frequency


$$\omega_c = \left(\frac{1}{RC}\right)\left(\frac{R + R_C}{R_C}\right)$$

- Maximum Amplitude if $j\omega=0$

$$|H(j\omega)|_{max} = \frac{R_C}{R + R_C}$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{1}{RC}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)\left(\frac{R + R_C}{R_C}\right)^2}}$$

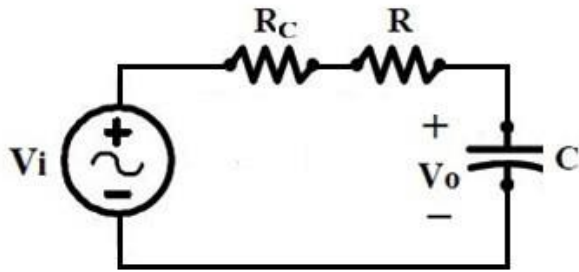F. RC CIRCUIT AND R_{load} SERIES


- Transfer function

$$H(s) = \frac{1}{s + \frac{1}{C(R + R_C)}}$$

- Cut-off frequency


$$\omega_c = \frac{1}{C(R + R_C)}$$

- Maximum Amplitude if $j\omega=0$

$$|H(j\omega)|_{max} = 1$$

II. HIGH PASS FILTER

A. RC CIRCUIT

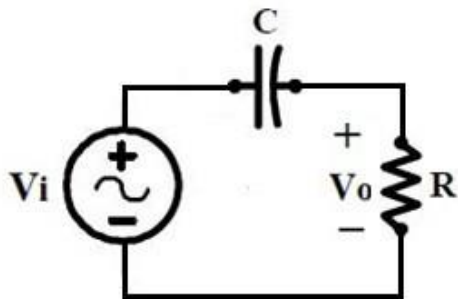

- Transfer function

$$H(s) = \frac{s}{s + \frac{1}{RC}}$$

- Cut-off frequency

$$\omega_c = \frac{1}{RC}$$

- Maximum Amplitude if $j\omega = \infty$

$$|H(j\omega)|_{max} = 1$$


- Angle

$$\theta(j\omega) = \frac{\pi}{2} - \tan^{-1}(\omega RC)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

B. RL CIRCUIT

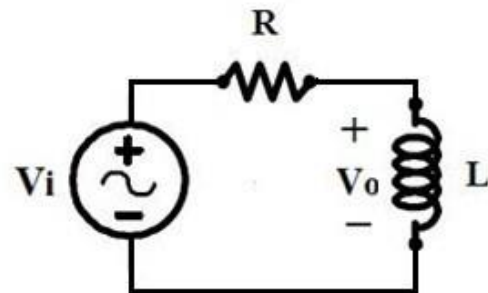

- Transfer function

$$H(s) = \frac{s}{s + \frac{R}{L}}$$

- Cut-off frequency

$$\omega_c = \frac{R}{L}$$

- Maximum Amplitude if $j\omega = \infty$


$$|H(j\omega)|_{max} = 1$$

- Angle

$$\theta(j\omega) = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega L}{R}\right)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

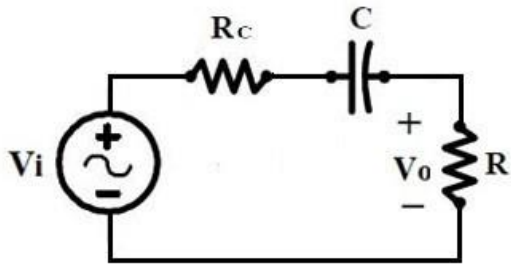
C. RC CIRCUIT AND R_{load} SERIES


- Cut-off frequency

$$\omega_c = \left(\frac{R}{L}\right)\left(\frac{R_L}{R + R_L}\right)$$

- Maximum Amplitude if $j\omega = \infty$

$$|H(j\omega)|_{max} = \frac{R_L}{R + R_L}$$

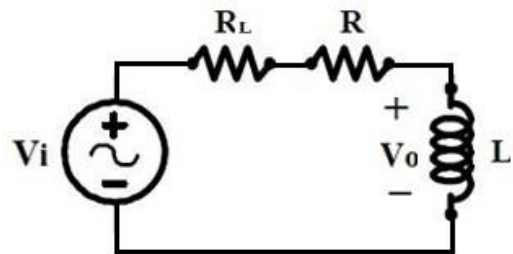 E. RL CIRCUIT AND R_{load} SERIES


- Transfer function


$$H(s) = \frac{S * \frac{R}{R + R_C}}{S + \frac{1}{C(R + R_C)}}$$

- Cut-off frequency

$$\omega_c = \frac{1}{C(R + R_C)}$$

- Maximum Amplitude if $j\omega = \infty$

$$|H(j\omega)|_{max} = \frac{R}{R + R_C}$$

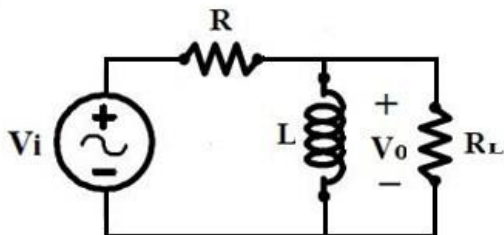 D. RL CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{S * \left(\frac{R_L}{R + R_L}\right)}{S + \left(\frac{R}{L}\right)\left(\frac{R_L}{R + R_L}\right)}$$

- Transfer function


$$H(s) = \frac{S}{S + \frac{R + R_L}{L}}$$

- Cut-off frequency

$$\omega_c = \frac{R + R_L}{L}$$

- Maximum Amplitude if $j\omega = \infty$

$$|H(j\omega)|_{max} = 1$$

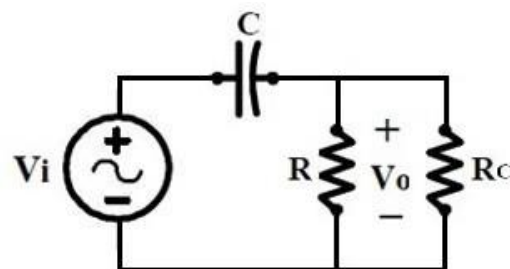 F. RC CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{S}{S + \left(\frac{1}{RC}\right)\left(\frac{R + R_C}{R_C}\right)}$$

- Cut-off frequency


$$\omega_c = \left(\frac{1}{RC}\right) \left(\frac{R + R_c}{R_c}\right)$$

- Maximum Amplitude if $j\omega = \infty$

$$|H(j\omega)|_{max} = 1$$

III. BAND PASS FILTER

A. SERIES RLC CIRCUIT

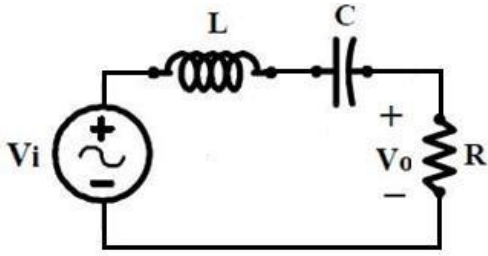

- Transfer function

$$H(s) = \frac{S \left(\frac{R}{L}\right)}{S^2 + S \left(\frac{R}{L}\right) + \frac{1}{RC}}$$

- Maximum Amplitude if $\omega = \omega_0$

$$|H(j\omega)|_{max} = 1$$

Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Angle

$$\theta(j\omega) = \frac{\pi}{2} - \tan^{-1} \left(\frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{\omega R}{L}}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{\omega R}{L}\right)^2}}$$


$$\begin{aligned} \omega_0 &= \sqrt{\omega_{c1} \omega_{c2}} \\ \omega_{c1} \text{ ó } \omega_{c2} &= \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)^2} \\ \beta &= \frac{R}{L} \text{ ó } \beta = \omega_{c1} - \omega_{c2} \end{aligned}$$

- Quality factor (Q)

$$Q = \sqrt{\frac{L}{CR^2}}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \omega_0 \left(\pm \frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right)$$

B. RLC CIRCUIT AND R_{load} SERIES

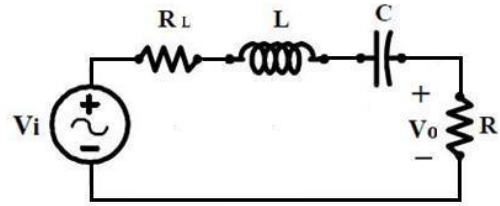

- Transfer function

$$H(s) = \frac{S \left(\frac{R}{L}\right)}{S^2 + S \left(\frac{R + R_L}{L}\right) + \frac{1}{RC}}$$

- Maximum Amplitude if $\omega = \omega_0$

$$|H(j\omega)|_{max} = \frac{R}{R + R_L}$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\frac{\omega R}{L}}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{\omega(R + R_L)}{L}\right)^2}}$$

$$\beta_u = \frac{R + R_L}{L}; \text{ with load}$$

$$\text{also } \beta = \omega_{c1} - \omega_{c2}$$



$$\beta = \frac{R_e}{L}; R_e = R + R_L$$

D. RLC CIRCUIT PARALLEL

- Quality factor (Q)

$$Q_u = \frac{\omega_0^2}{R + R_L}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{R + R_L}{2L} + \sqrt{\omega_0^2 + \left(\frac{R + R_L}{2L}\right)^2}$$

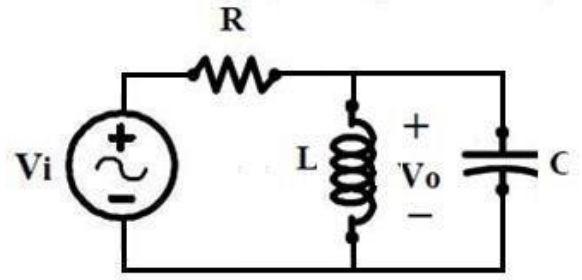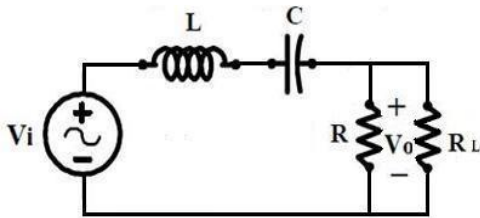
 C. RLC CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{S \left(\frac{R}{L}\right) \left(\frac{R_L}{R + R_L}\right)}{S^2 + S \left(\frac{R}{L}\right) \left(\frac{R + R_L}{L}\right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = \omega_0$

$$|H(j\omega)|_{max} = 1$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta_u = k\beta ; \text{with load}$$

where $\beta = \omega_{c1} - \omega_{c2}$

$$\beta = \frac{R}{L} ; k = \frac{R}{R + R_L}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{\beta_u}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta_u}{2}\right)^2}$$

- Transfer function

$$H(s) = \frac{S \left(\frac{1}{RC}\right)}{S^2 + S \left(\frac{1}{RC}\right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = \omega_0$

$$|H(j\omega)|_{max} = 1$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Angle

$$\theta(j\omega) = \frac{\pi}{2} - \tan^{-1} \left(\frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right)$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{\omega \left(\frac{1}{RC}\right)}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{\omega}{RC}\right)^2}}$$


$$\beta = \frac{1}{RC}$$

$$\text{also } \beta = \omega_{c1} - \omega_{c2}$$

- Quality factor (Q)

$$Q = \sqrt{\frac{R^2 C}{L}}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \left(\frac{1}{LC}\right)^2}$$

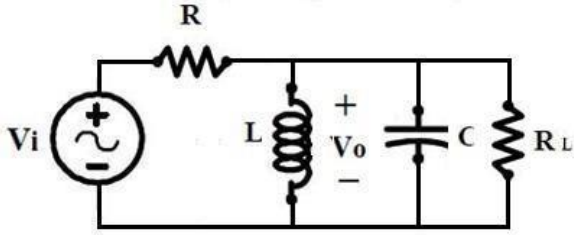E. RLC CIRCUIT AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{s \left(\frac{1}{RC} \right) \left(\frac{R + R_L}{R} \right) \left(\frac{R}{R + R_L} \right)}{s^2 + s \left(\frac{1}{RC} \right) \left(\frac{R + R_L}{R_L} \right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = \omega_0$

$$|H(j\omega)|_{max} = 1$$

Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta_u = \left(\frac{1}{RC} \right) \left(\frac{R + R_L}{R_L} \right); \text{ with load}$$

also $\beta = \omega_{c1} - \omega_{c2}$

$$\beta = \frac{1}{RC} \rightarrow \beta_u = \left(1 + \frac{R}{R_L} \right) \beta$$

- Rewriting $H(s = j\omega)$

$$H(s = j\omega) = \frac{\omega \left(\frac{R}{L} \right)}{\sqrt{\left(\frac{1}{LC} - \omega^2 \right)^2 + \left(\frac{\omega(R + R_L)}{L} \right)^2}}$$


- Quality factor (Q)

$$Q = \frac{\omega_0}{\beta}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{\beta}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta}{2} \right)^2}$$

IV. BAND REJECT FILTER

A. RLC SERIES CIRCUIT

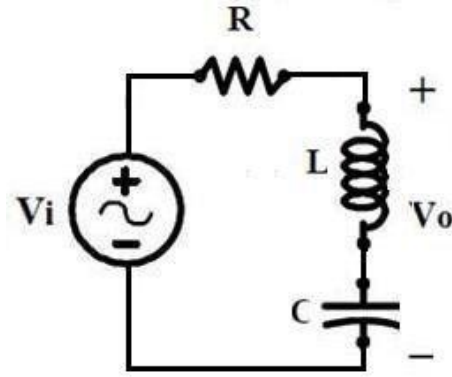

- Transfer function

$$H(s) = \frac{s^2 + \left(\frac{1}{LC} \right)}{s^2 + s \left(\frac{R}{L} \right) + \frac{1}{LC}}$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Angle

$$\theta(j\omega) = -\tan^{-1} \left(\frac{\frac{\omega R}{L}}{\frac{1}{LC} - \omega^2} \right)$$

- Amplitude of $H(j\omega)$


$$|H(j\omega)| = \frac{\left| \frac{1}{LC} - \omega^2 \right|}{\sqrt{\left(\frac{1}{LC} - \omega^2 \right)^2 + \left(\frac{\omega R}{L} \right)^2}}$$

$$\beta = \frac{R}{L} \text{ ó } \beta = \omega_{c1} - \omega_{c2}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{\beta}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta}{2} \right)^2}$$

- Quality factor (Q)

$$Q = \sqrt{\frac{L}{R^2 C}}$$

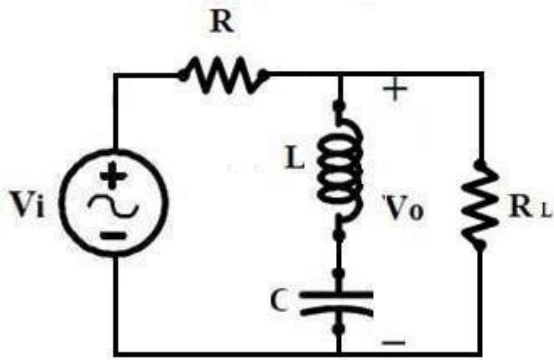B. LC SERIES. R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{\left(s^2 + \frac{1}{LC}\right) \left(\frac{R_L}{R + R_L}\right)}{s^2 + s\left(\frac{R}{L}\right)\left(\frac{R_L}{R + R_L}\right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = 0$ ó $\omega = \infty$

$$|H(j\omega)|_{max} = k$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{So } k = \frac{R_L}{R + R_L}$$

$$\beta = \frac{R_e}{L} \text{ where } R_e = \frac{RR_L}{R + R_L}$$

- Rewriting $H(s)$


$$H(s) = \frac{k(s^2 + \omega^2)}{s^2 + \beta_u s + \omega_0^2}$$

$$-\omega_{c1} \text{ ó } \omega_{c2} == \pm \frac{\beta}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta}{2}\right)^2}$$

- Quality factor (Q)

$$Q = \left(\frac{R + R_L}{R_L}\right) \left(\frac{\omega_0 L}{R}\right)$$

C. RLC CIRCUIT. LC PARALLEL

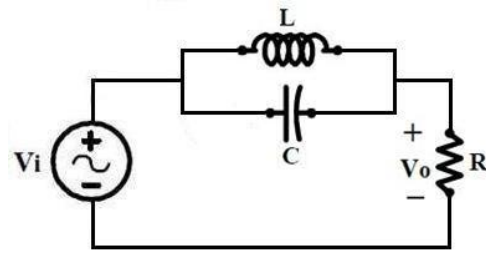

- Transfer function

$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + s\left(\frac{1}{RC}\right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = 0$ ó $\omega = \infty$

$$|H(j\omega)|_{max} = 1$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \frac{1}{RC}$$

- Rewriting $H(s)$

$$H(s) = \frac{s^2 + \omega^2}{s^2 + \beta s + \omega_0^2}$$


- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{|\omega_0^2 - \omega^2|}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\beta)^2}}$$

$$\omega_{c1} \text{ ó } \omega_{c2} == \pm \frac{\beta}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta}{2}\right)^2}$$

- Quality factor (Q)

$$Q_u = \omega_0 RC$$

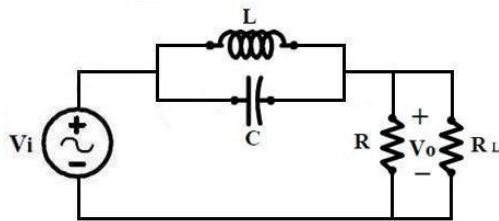D. RLC CIRCUIT, LC PARALLEL AND R_{load} PARALLEL


- Transfer function

$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + s\left(\frac{1}{RC}\right)\left(\frac{R + R_L}{R}\right) + \frac{1}{LC}}$$

- Maximum Amplitude if $\omega = 0$ ó $\omega = \infty$

$$|H(j\omega)|_{max} = 1$$

- Where ω_0 is defined as

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \frac{\omega_0}{R_e C}$$

$$R_e = \frac{RR_L}{R + R_L}$$

- Rewriting $H(s)$

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

- Amplitude of $H(j\omega)$

$$|H(j\omega)| = \frac{|\omega_0^2 - \omega^2|}{\sqrt{(\omega_0^2 - \omega^2)^2 + (\omega\beta)^2}}$$

$$\omega_{c1} \text{ ó } \omega_{c2} = \pm \frac{\beta}{2} + \sqrt{\omega_0^2 + \left(\frac{\beta}{2}\right)^2}$$

- Quality factor (Q)

$$Q = \omega_0 R_e C$$