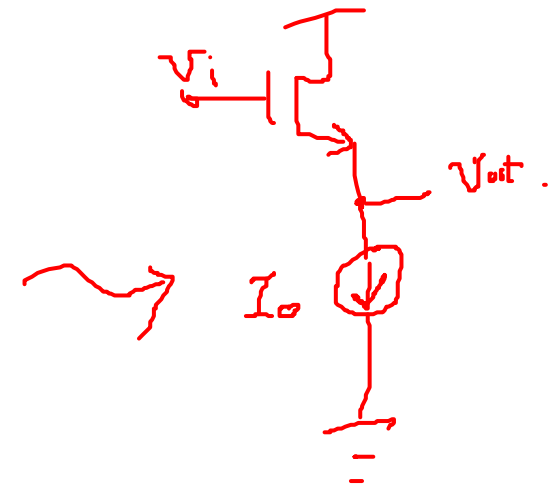


Current Mirrors




Javier Ardila

Integrated Systems Research Group – OnChip

Universidad Industrial de Santander, Bucaramanga - Colombia



javier.ardila@e3t.uis.edu.co

Universidad
Industrial de
Santander

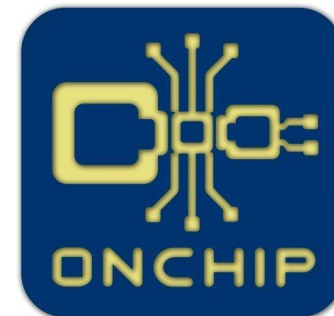

Current Source Properties

➤ Output resistance:

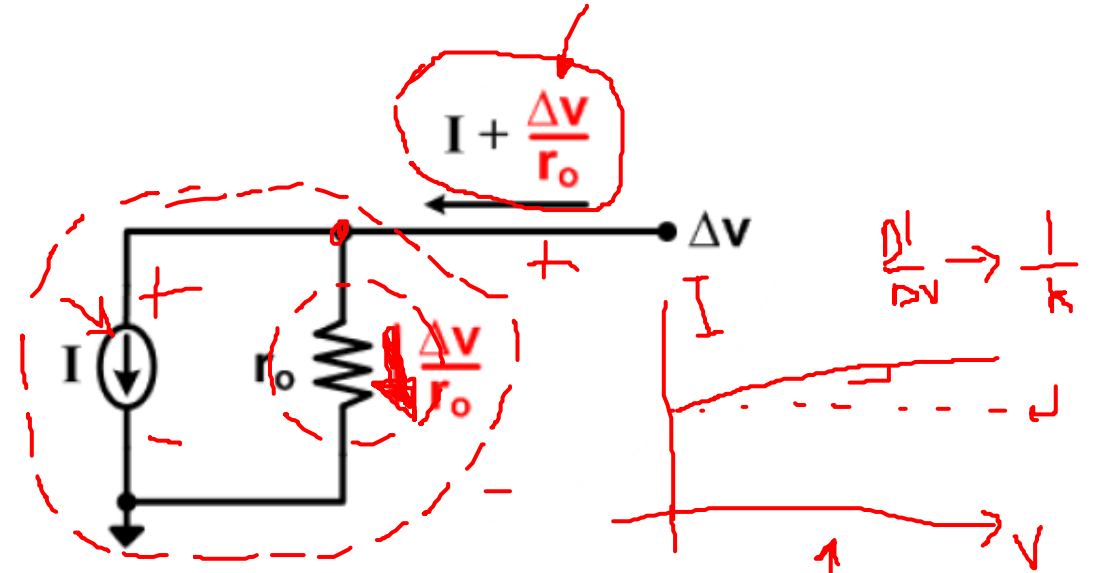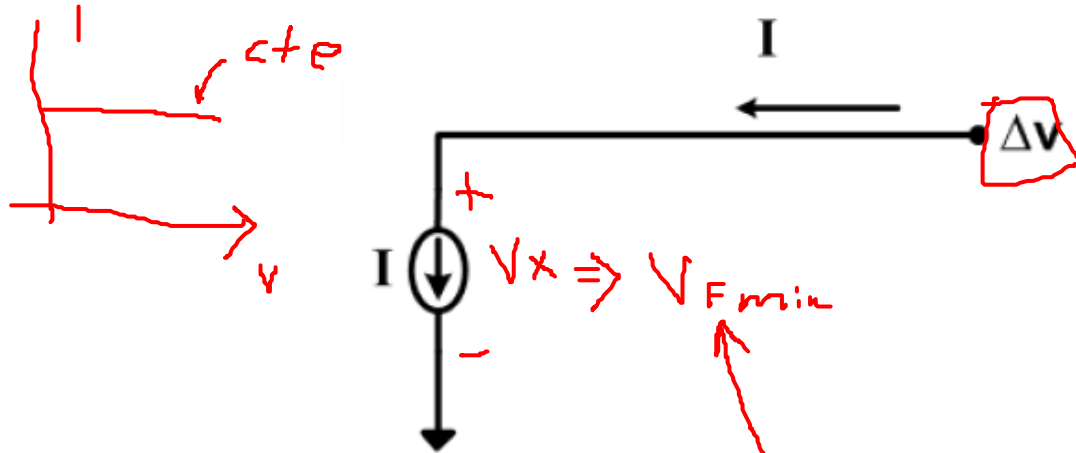

➤ Finite output resistance degrades current source accuracy and amplifier gain.


➤ Other important properties:

- Compliance voltage (headroom voltage in this case) → maximum voltage that the current source can supply to a load.


- Accuracy

→ C_{opias}

- Noise

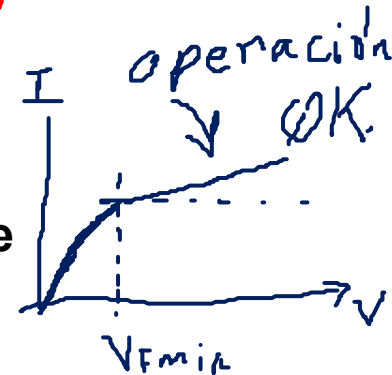


Circuits Biasing Issues

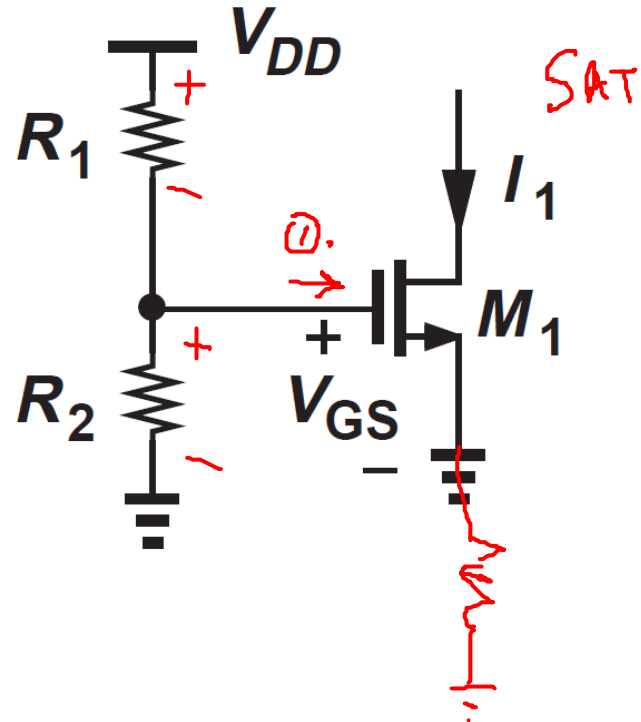

$$\begin{aligned} I_1 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \end{aligned}$$


- Assuming saturation, I_D is sensitive to: supply (V_{DD}), process (V_{TH} & $\mu_n C_{ox}$) and Temperature (V_{TH} & μ_n). So this is not a good biasing.

High-Accuracy Current Sources

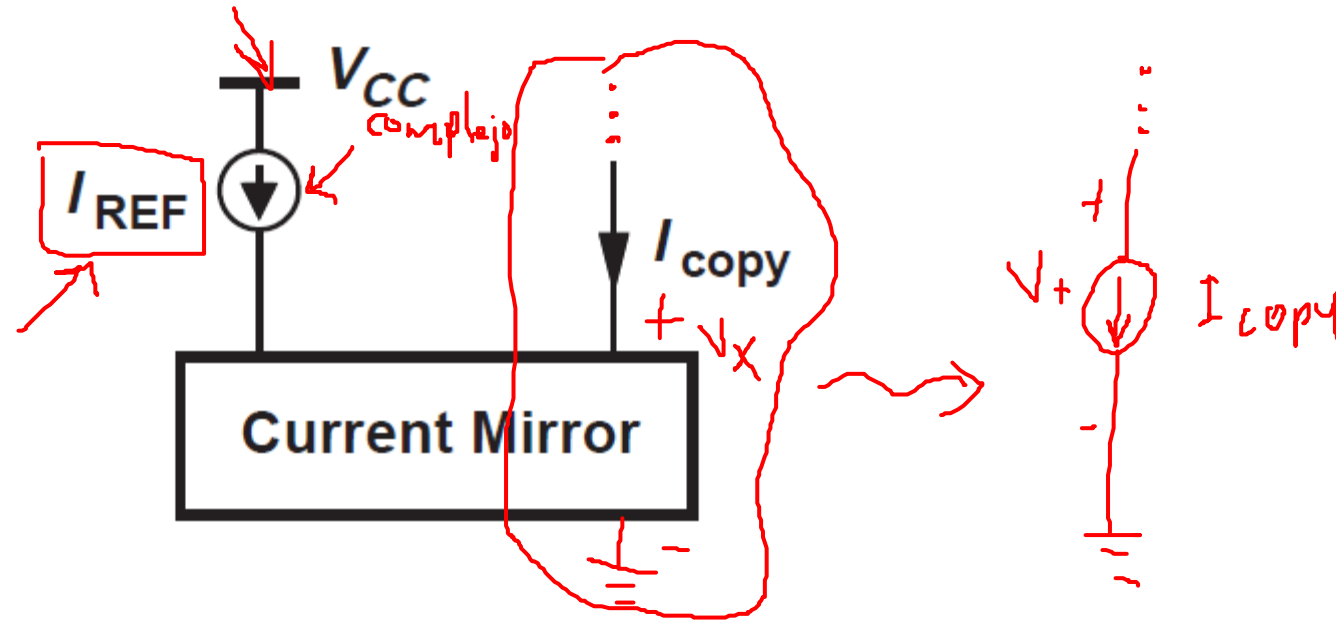

- Generating a high-accuracy current source (I_{REF}) is possible through a “bandgap reference” circuit, which employs several tens of devices to generate a supply-, process- and temperature-independent voltage.
- However, putting I_{REF} wherever it's needed implies a high cost in terms of area.


Current Mirror as a Solution

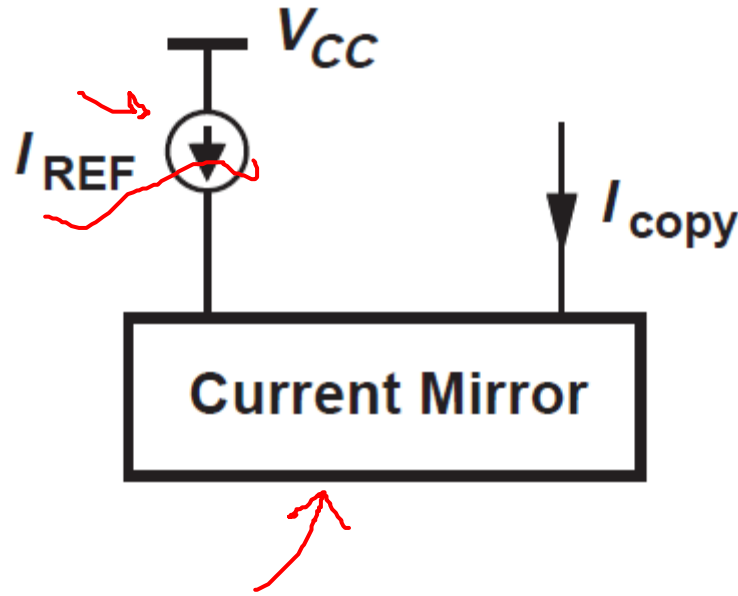

- Given the area problems, generating only one I_{REF} and copying its current value to wherever it's necessary rises as a possible solution.

How to copy current?

$\lambda=0$

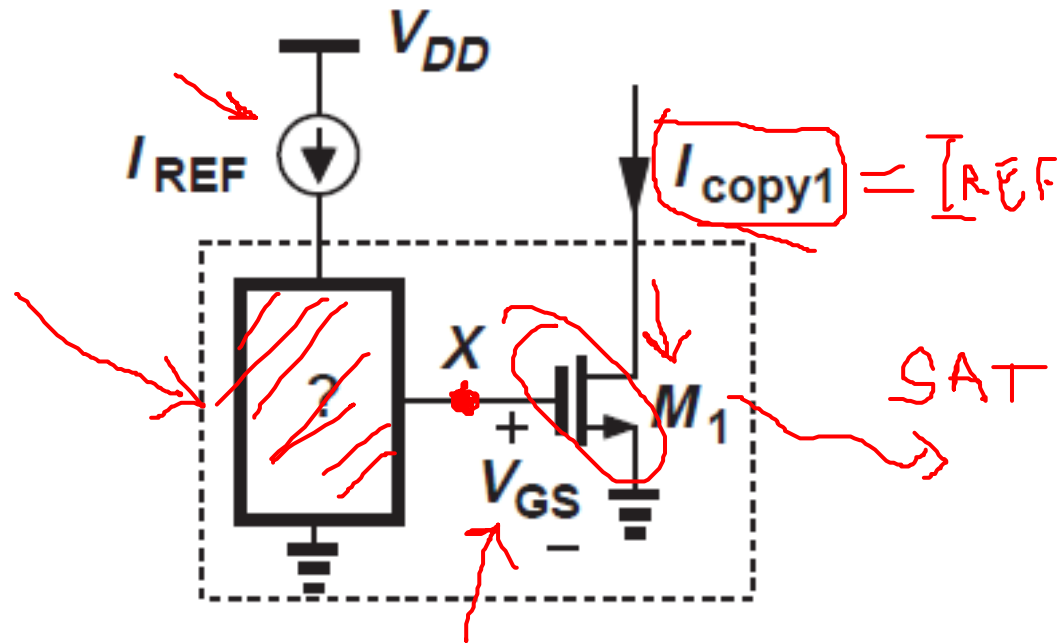


$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_X - V_{TH1})^2 = I_{REF}$$

➤ What should the black box be so that $I_{REF} \approx I_{copy1}$?



Simple Current Mirror

$\lambda=0$

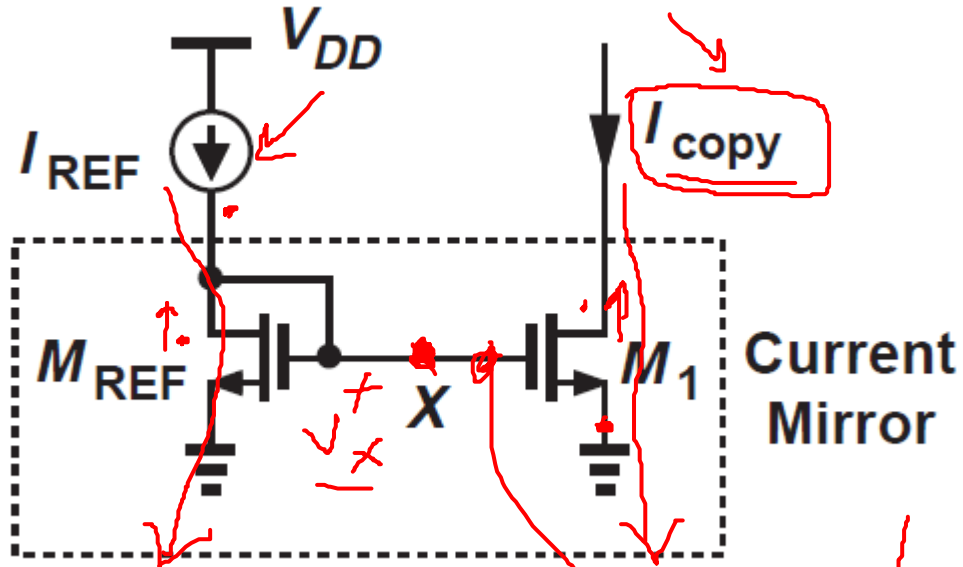

Si $M_1 = M_{REF}$

$\rightarrow I_{D,REF} \approx I_{copy}$ if $(W/L)_{REF} = (W/L)_1$


SAT

$$I_{D,REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{REF} (V_X - V_{TH})^2$$

$$I_{copy} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_X - V_{TH})^2$$

$$I_{copy} = \frac{\left(\frac{W}{L} \right)_1}{\left(\frac{W}{L} \right)_{REF}} I_{REF}$$

Current Multiplication With CMs

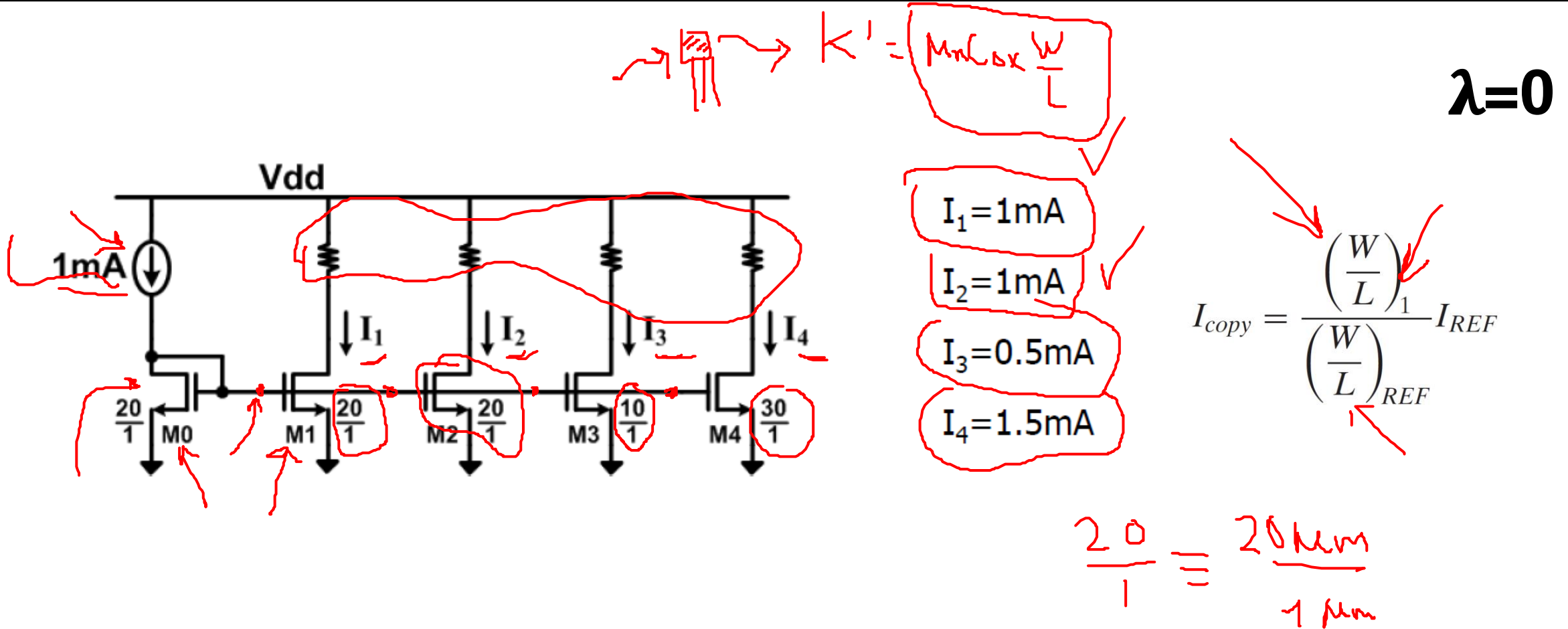


- Next time: What happens if we consider $\lambda=0$?
- Are there more current mirror configurations?


Additional points!!! - Design Exercise

- In 10min, design a current mirror that produces I_1 and I_2 from an I_{REF} of 0.3mA.

$$\lambda=0$$

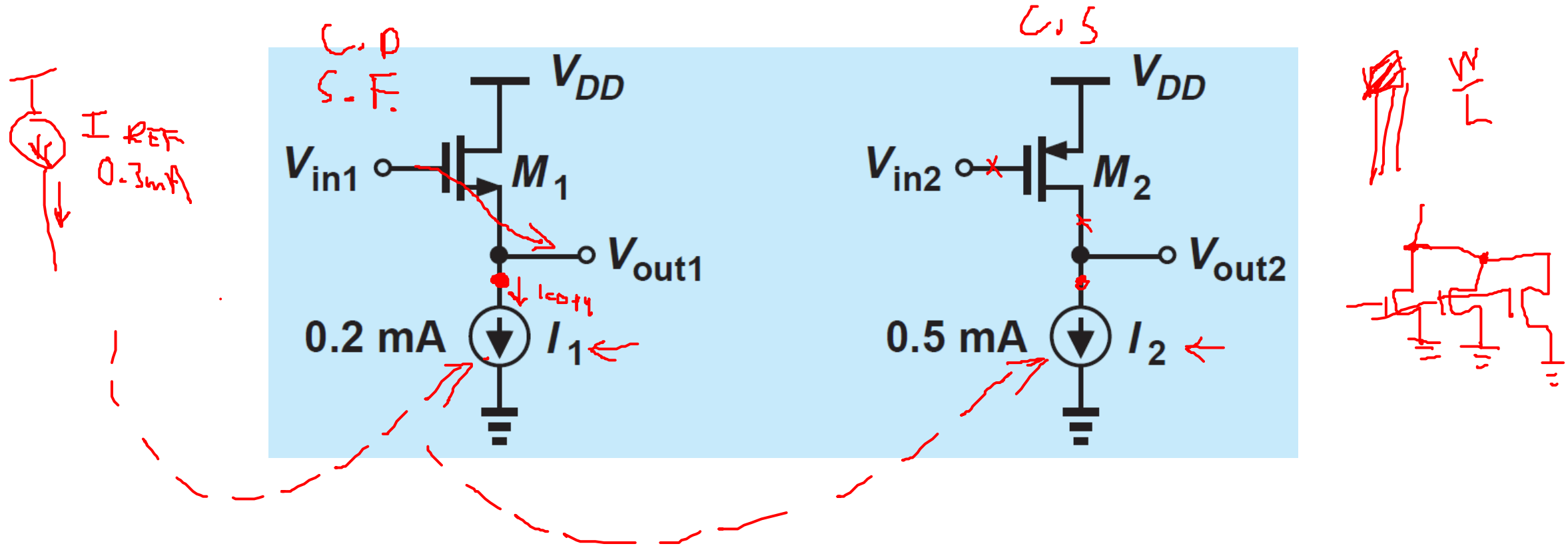

Accuracy Limitations of Simple CMs

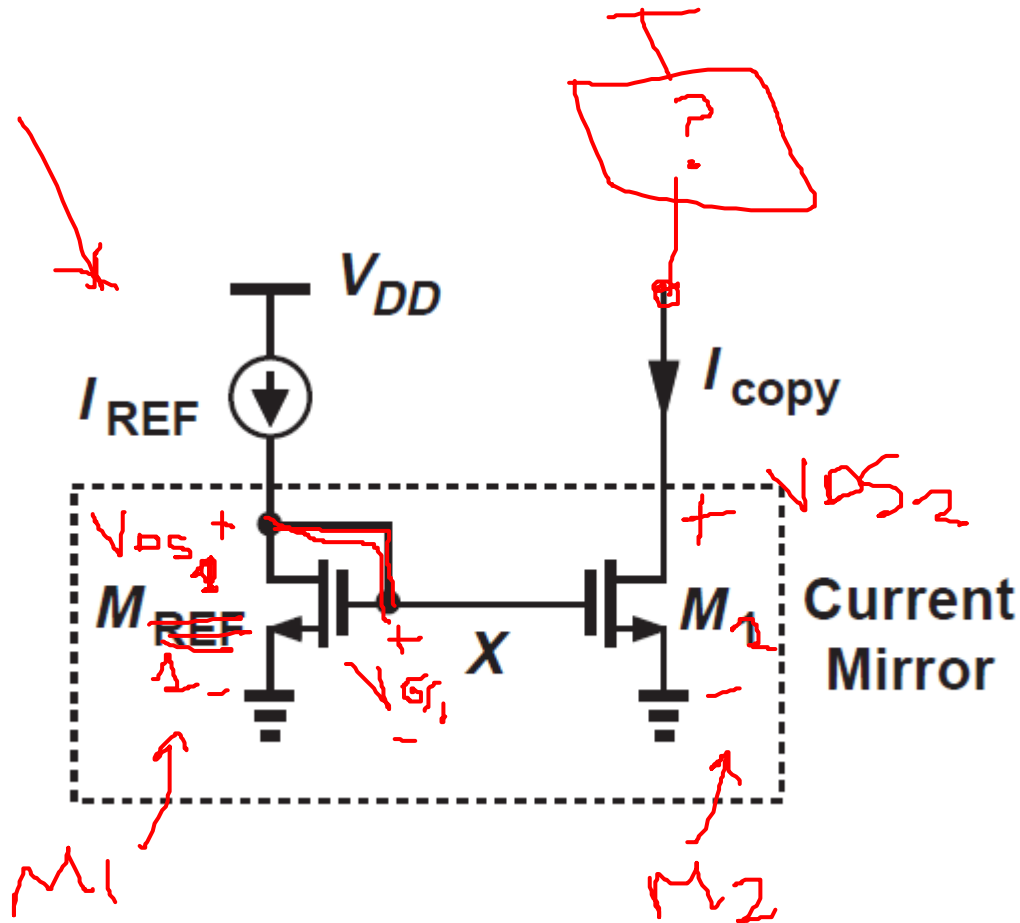

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS1})$$


$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS2})$$

$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

- Channel-length modulation induces inaccuracy in simple current mirrors.

Accuracy Limitations of Simple CMs

③

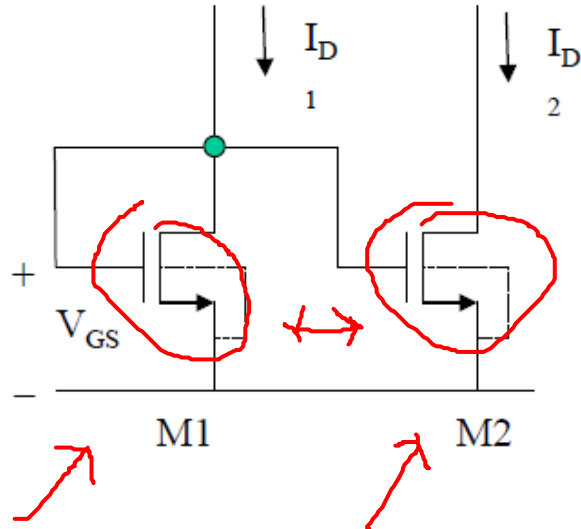

In general $(W/L)_2 = N(W/L)_1$, most probably $V_{T1} \neq V_{T2}$, then

$$I_{D2} = \frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_2 (V_{GS} - V_T)^2 (1 + \lambda_2 V_{DS2})$$

$$I_{D2} = \frac{\frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{T2})^2 (1 + \lambda_2 V_{DS2})}{\frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{T1})^2 (1 + \lambda_1 V_{DS1})} I_{D1} = \frac{K_{P2} (V_{GS} - V_{T2})^2 (1 + \lambda_2 V_{DS2})}{K_{P1} (V_{GS} - V_{T1})^2 (1 + \lambda_1 V_{DS1})} N I_{D1}$$

$$\text{Error} \approx \lambda_2 V_{DS2} \neq \lambda_1 V_{DS1}$$

$$\lambda \propto \frac{1}{L}$$

Long devices reduce the error; make $V_{DS1} = V_{DS2}$

$$\text{Error} \approx K_{P2} \neq K_{P1}$$


Errors can be reduced (but not eliminated) by using replicas of the main device and good layout!

$$\text{Error} \approx V_{T2} \neq V_{T1}$$

Effective mobility and threshold voltages are sensitive to V_{DS} and V_{dsat}


Good solution ==> use cascode structures

How to equal V_{DS1} and V_{DS2} ?

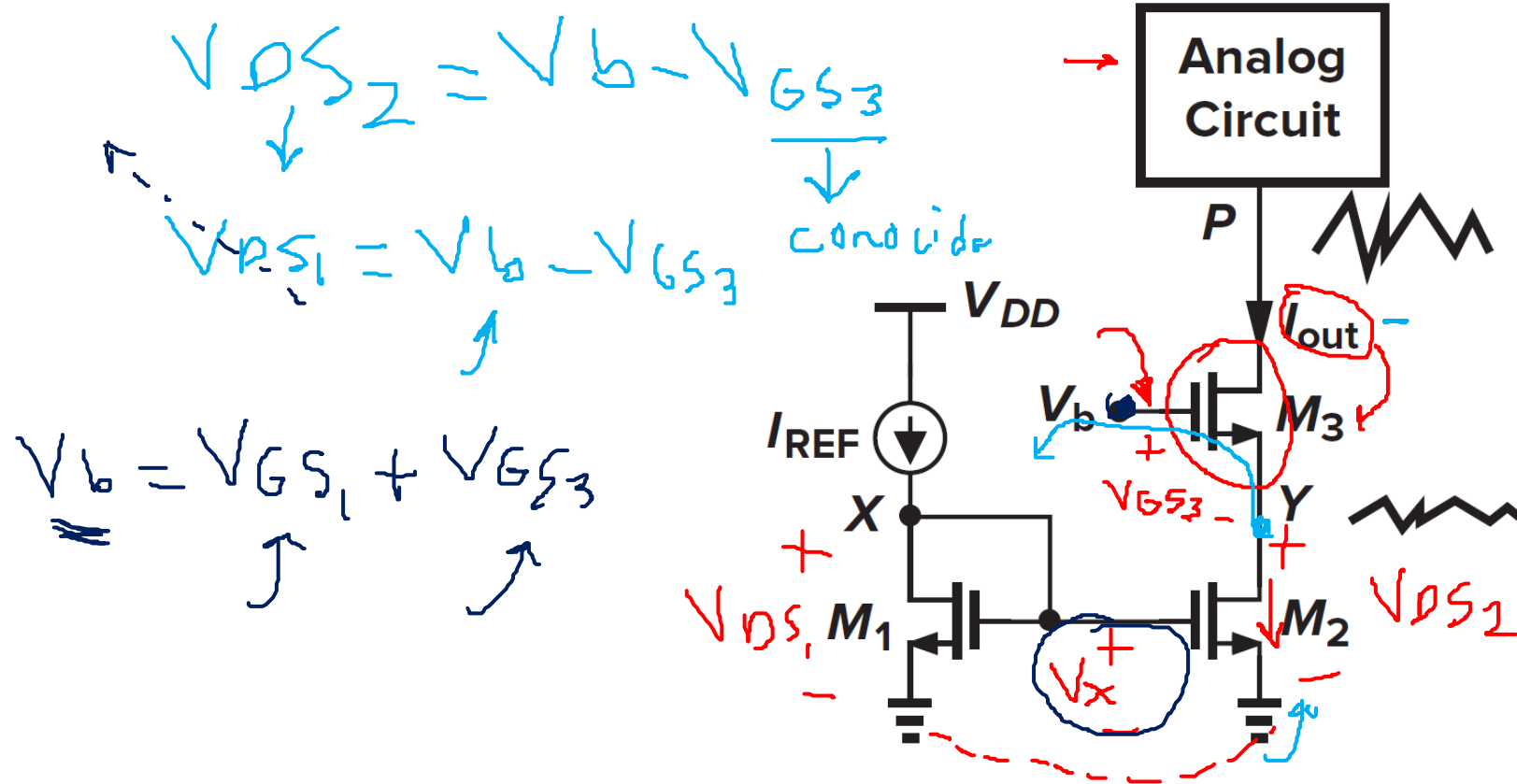


- M_3 shields node Y from variations in P , thus keeping node Y *relatively constant*.
- Generate V_b such that $V_{S3} = V_b - V_{GS3} = V_{DS1}$, which means $V_b = V_{GS3} + V_{DS1}$.

How to generate V_b ?

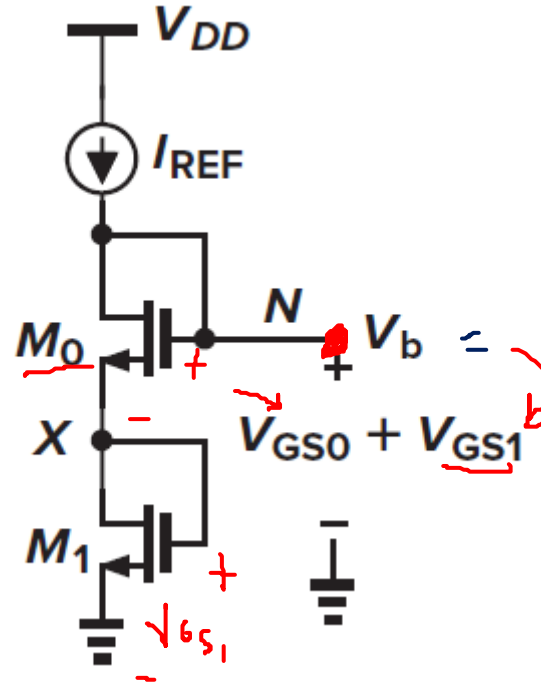

- $V_b = V_{GS3} + V_{DS1}$ means that V_b can be generated from two diode-connected transistors.
- In this case, $V_{GS0} = V_{GS3}$.


Cascode Current Mirror

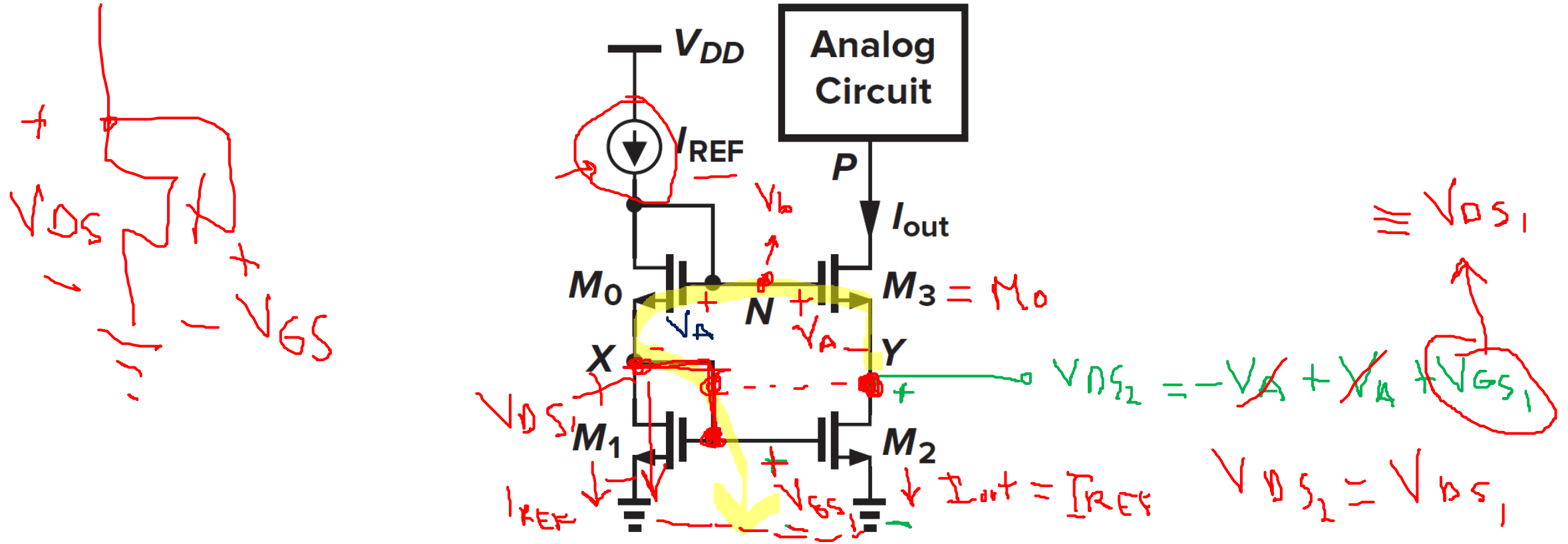


- Therefore, a cascode current mirror allows generating an accurate current copy at I_{out} .

Trouble in Paradise?
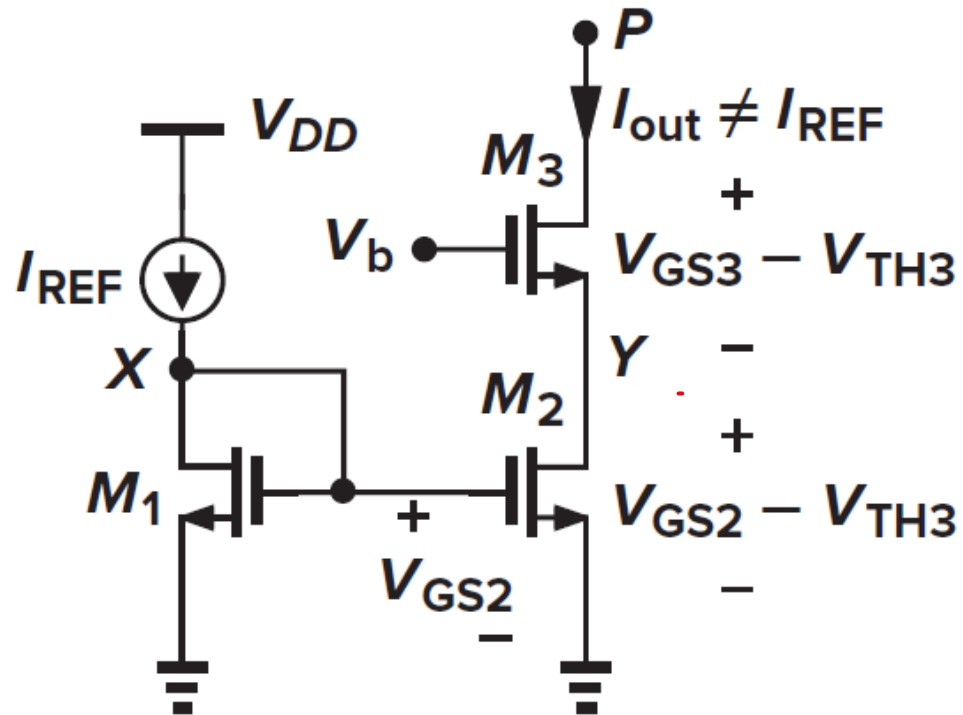
$$V_P = (V_{GS3} - V_{TH}) + (V_{GS2} - V_{TH}) = 2V_{OV}$$




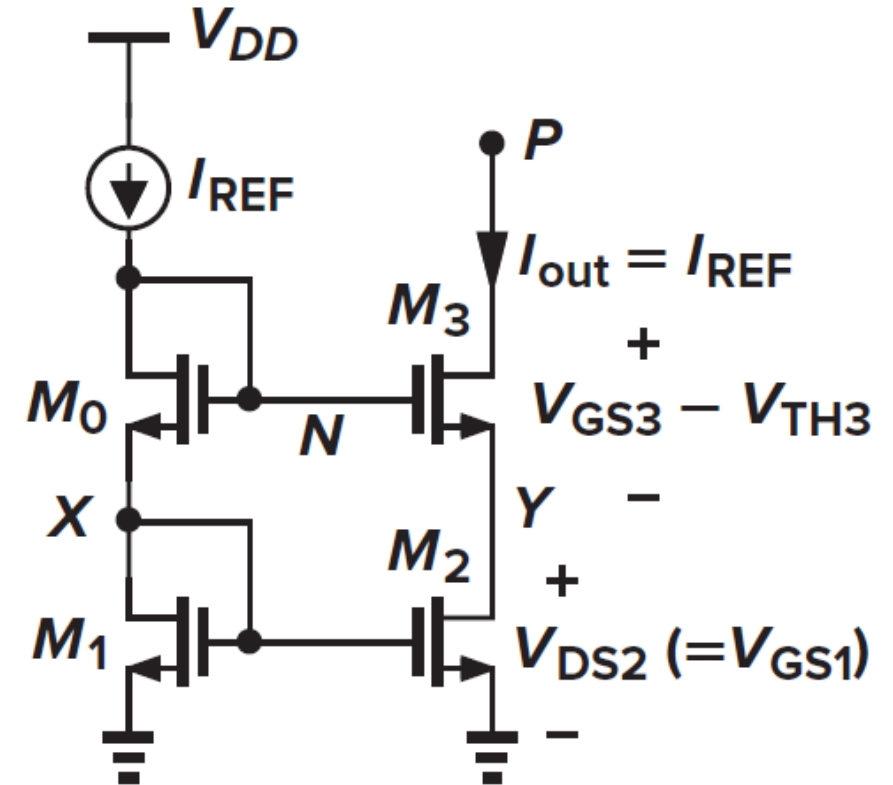
$$V_P = (V_{GS3} - V_{TH}) + (V_{GS1}) = 2V_{OV} + V_{TH}$$




- While operating with a high output impedance value and an accurate current, the cascode CM consumes significant voltage headroom.

Comparing Simple and Cascode CMs

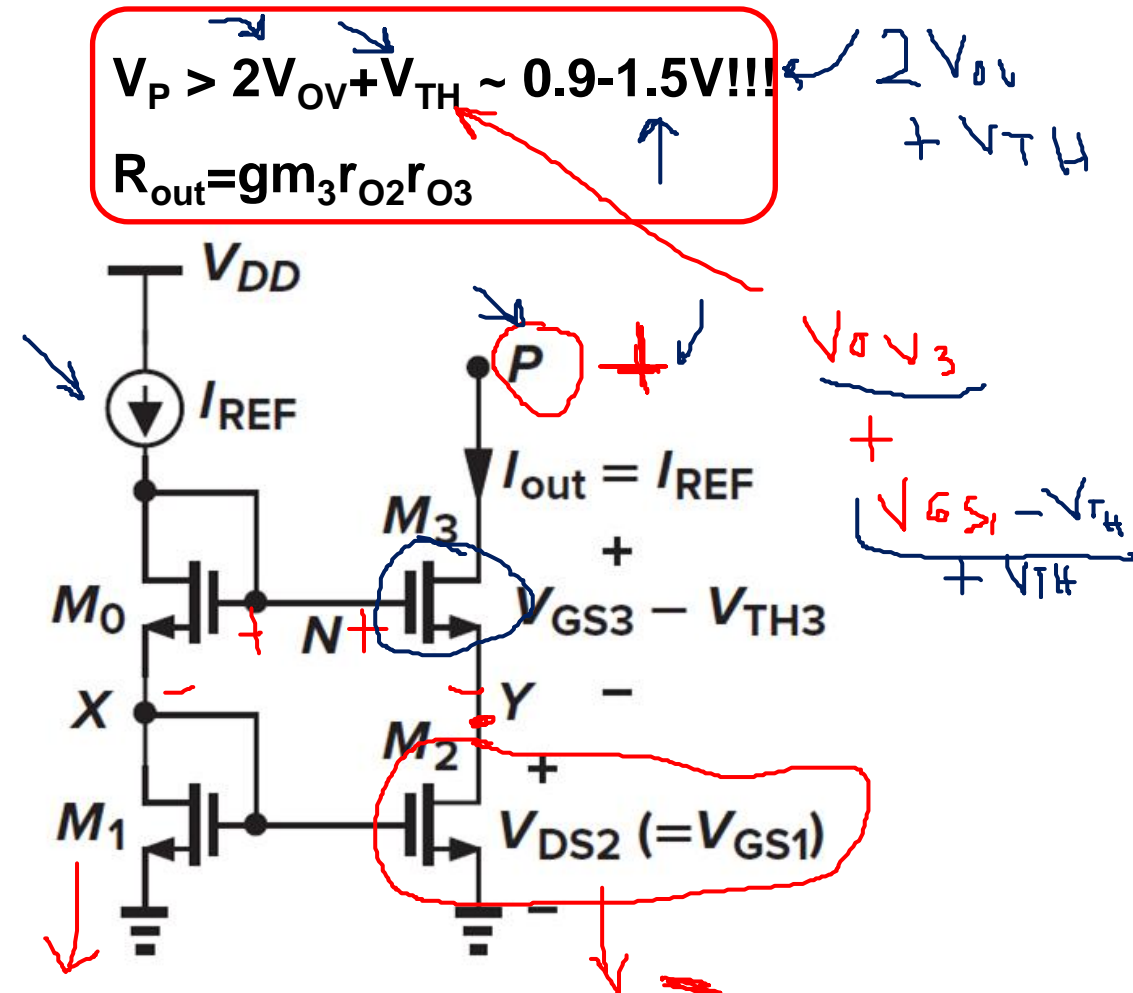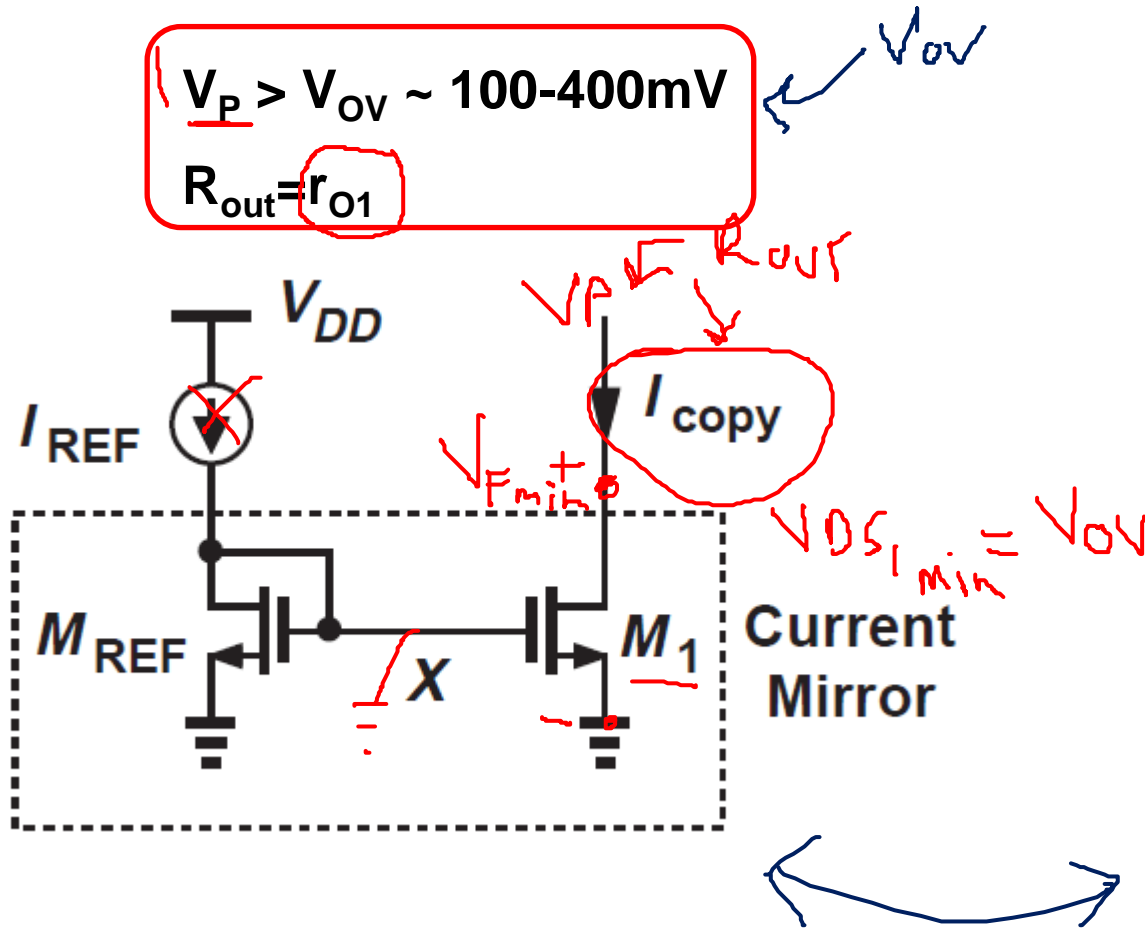

- While operating with a high output impedance value and an accurate current, the cascode CM consumes significant voltage headroom.


Solution?

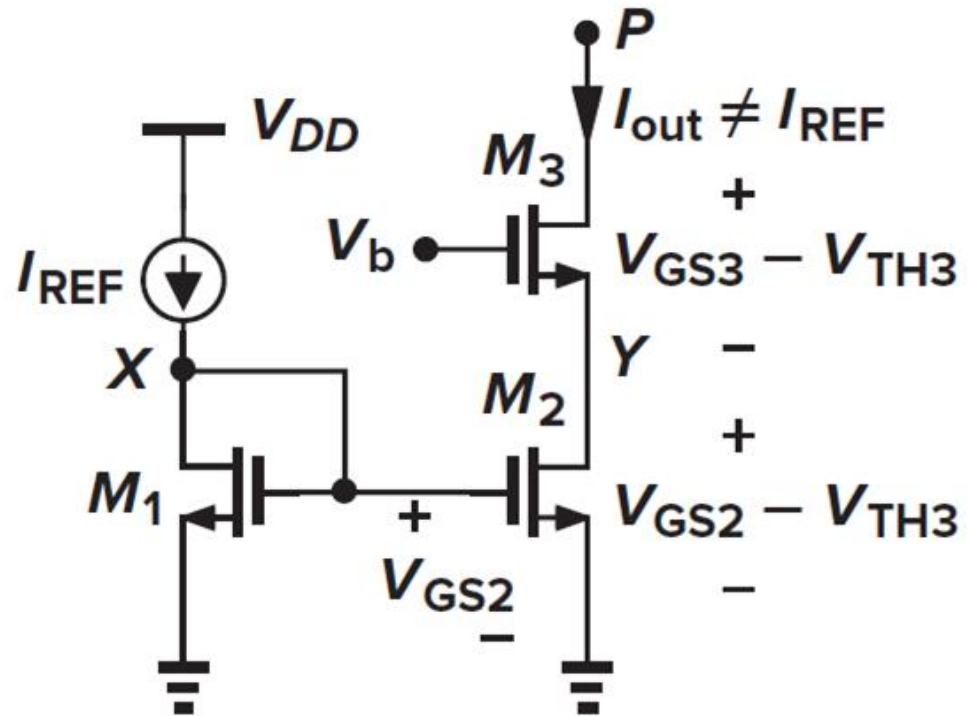

The headroom issue would be mitigated if $V_b = V_{GS3} + (V_{GS2} - V_{TH})$, i.e., $V_{DS2} \sim V_{OV}$

- Instead of forcing V_{DS2} equal to V_{GS1} , which causes problems, we can force V_{GS1} equal to V_{DS2} .


An Intuitive Modification

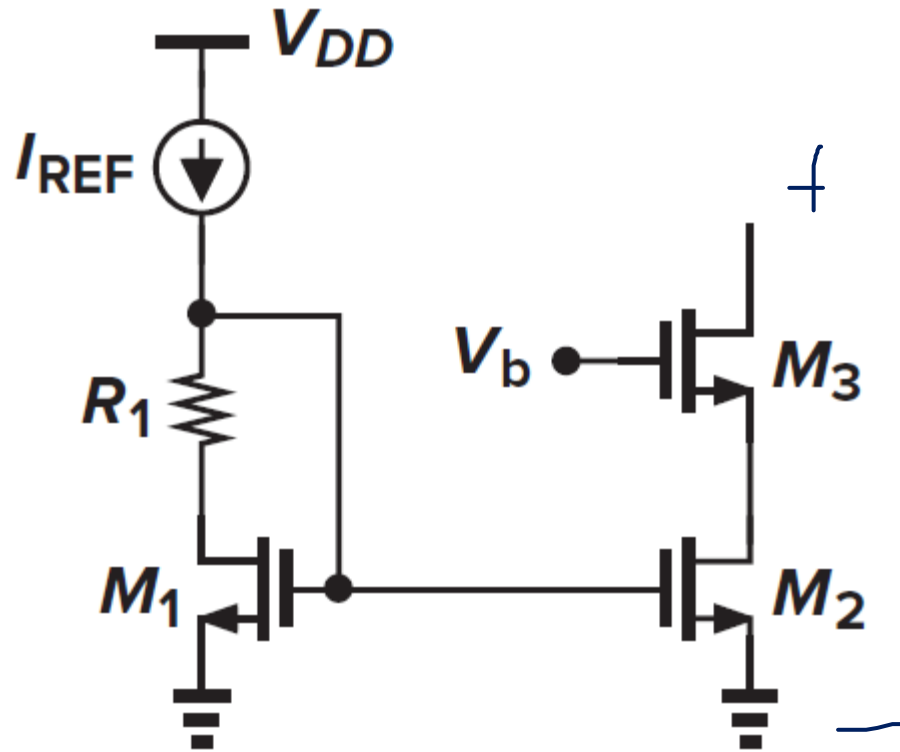

If $I_{REF} \cdot R_1 = V_{TH}$ and $V_b = V_{GS3} + (V_{GS1} - V_{TH})$, we can ensure $V_{DS1} = V_{DS2} = V_{OV}$

- Instead of forcing V_{DS2} equal to V_{GS1} , which causes problems, we can force V_{GS1} equal to V_{DS2} .

Avoiding PVT Variations on Resistor

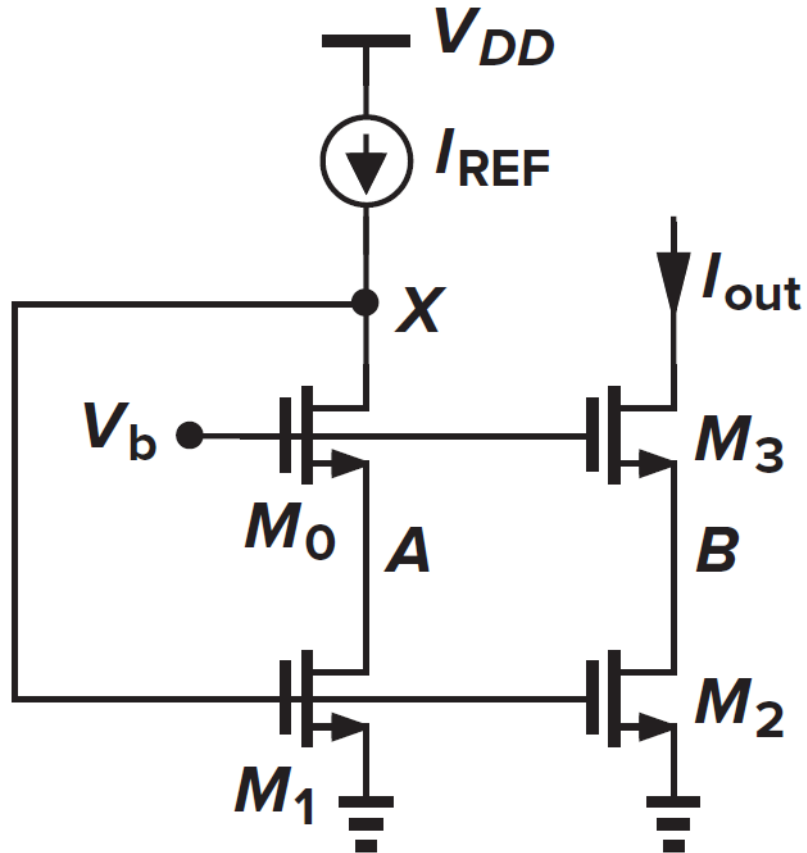


If $V_{GS0}=V_{GS3}$, we can ensure $V_{DS1}=V_{DS2}=V_b - V_{GS0,3}$

under some conditions:

1. $V_{GS0} - V_{TH} < V_{TH}$
2. $V_b = V_{GS0} + (V_{GS1} - V_{TH})$

➤ Instead of forcing V_{DS2} equal to V_{GS1} , which causes problems, we can force V_{GS1} equal to V_{DS2} .

Accomplishing Conditions

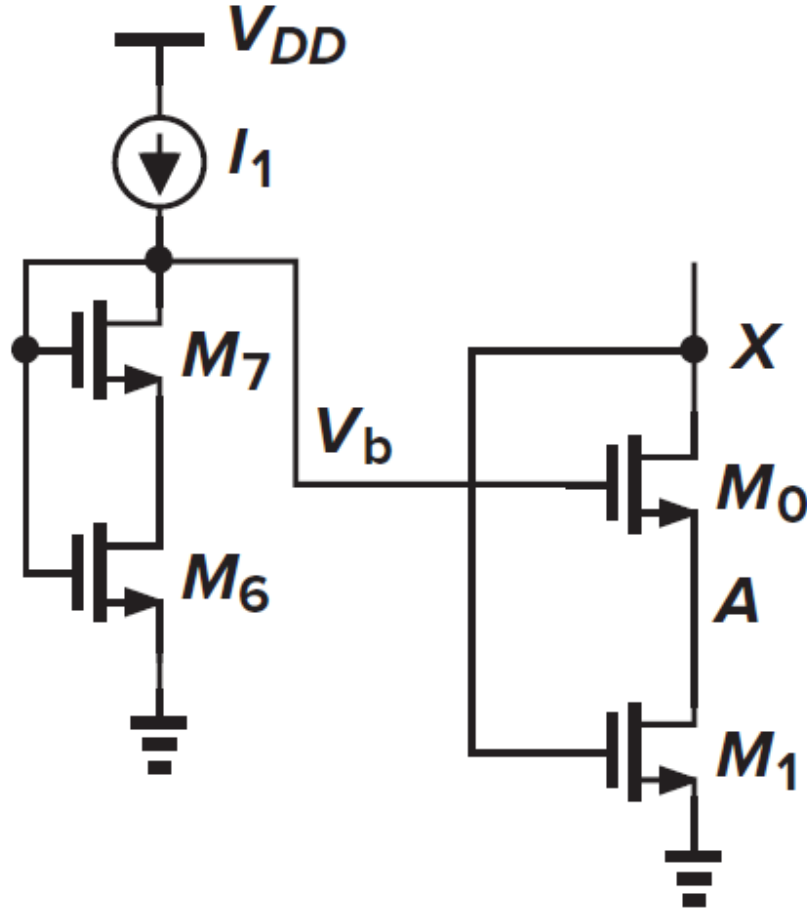


If $V_{GS0}=V_{GS3}$, we can ensure $V_{DS1}=V_{DS2}=V_b - V_{GS0,3}$

under some conditions:

1. $V_{GS0} - V_{TH} < V_{TH} \rightarrow M_0$ Sizing
2. $V_b = V_{GS0} + (V_{GS1} - V_{TH}) \rightarrow$ This topology

➤ $V_b = V_{GS7} + (V_{GS6} - V_{TH})$, $V_{GS7} = V_{GS0}$, $V_{GS6} = V_{GS1}$. This topology produces a headroom of $2V_{OV}$.



Exercise - CMs in Typical Circuits

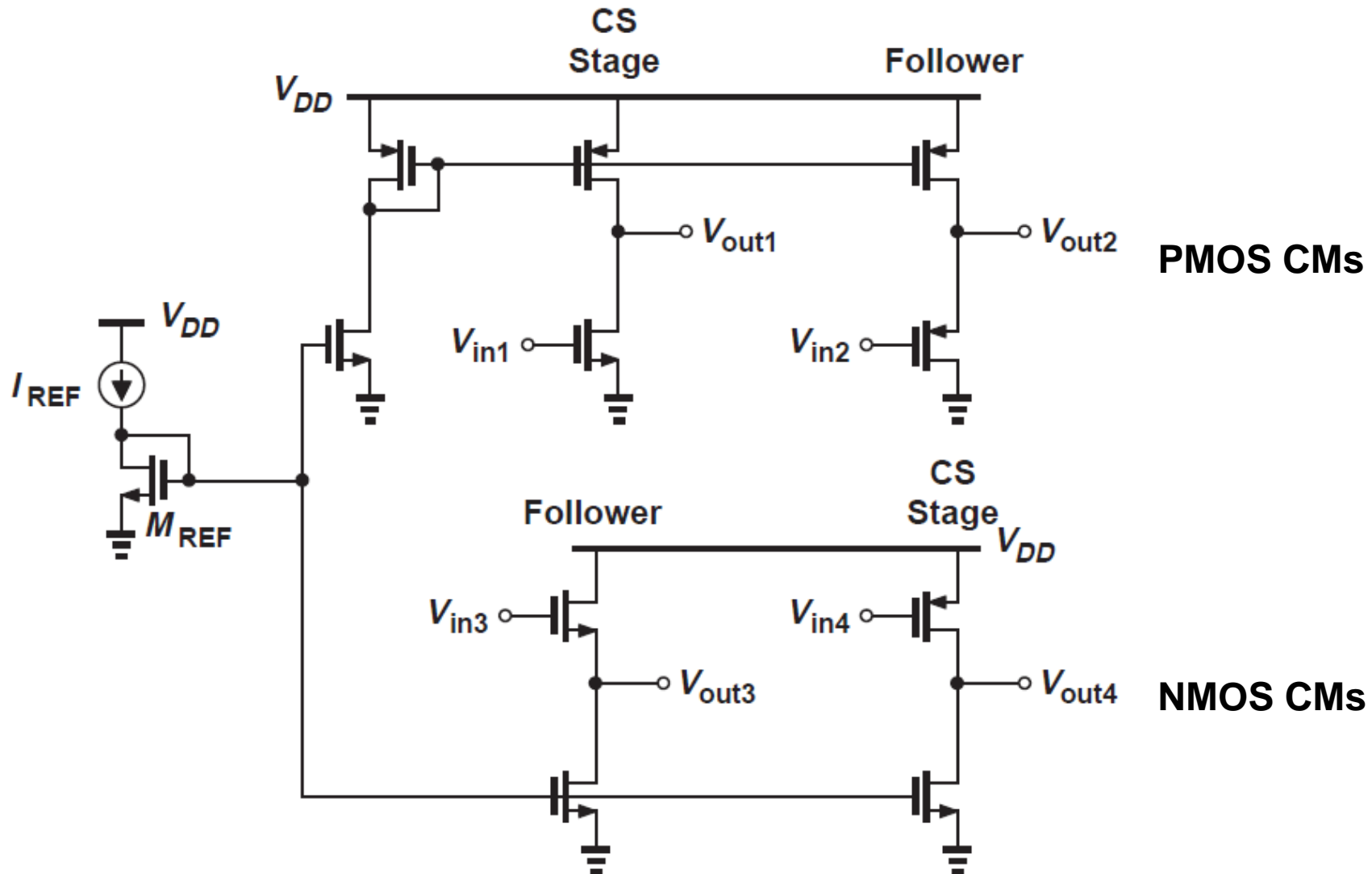

Thanks



javier.ardila@correo.uis.edu.co

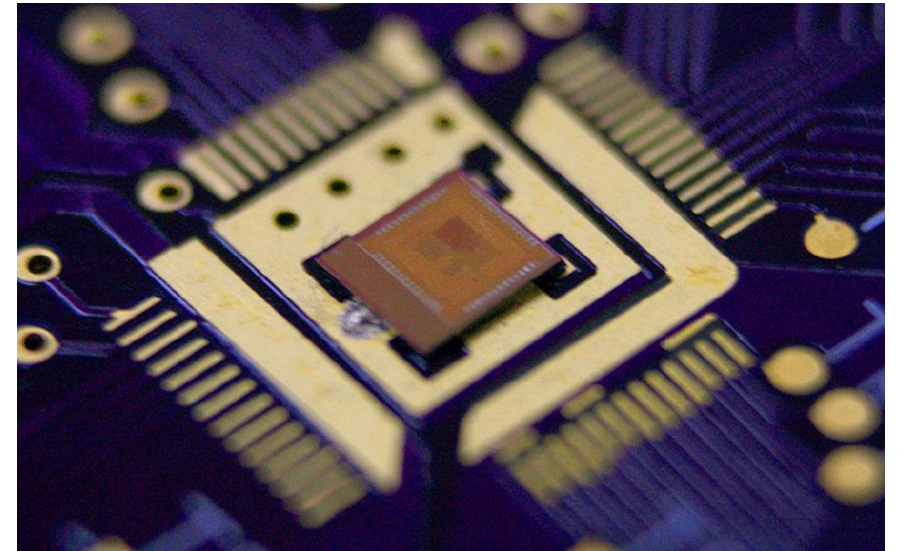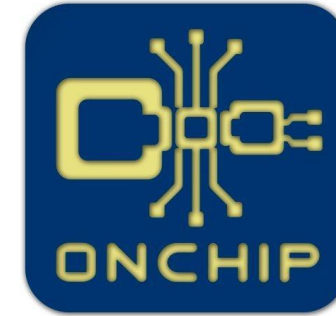

@onchipUIS