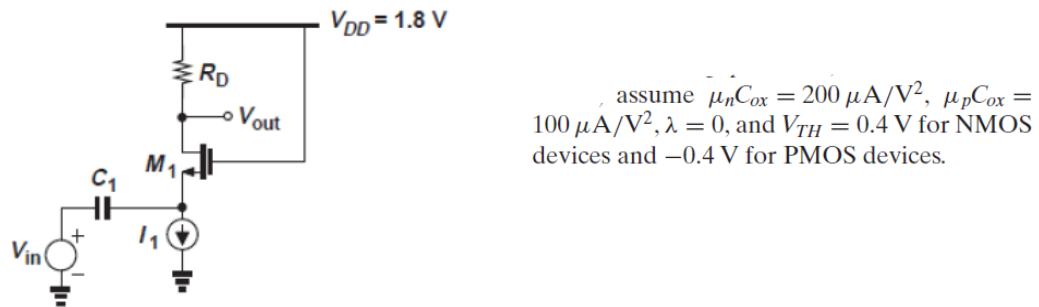



**Foundations of Analog Circuits**  
**Semester 2021-2**  
**Problem Set – EXAM 1**  
**Prof. Javier Ardila & David Reyes**

1. The CG amplifier shown below, is biased by means of  $I_1 = 1\text{mA}$ . Assume  $\lambda=0$  and  $C_1$  is very large. A) What value of  $R_D$  places the transistor  $M_1$  100mV away from the triode region? B) What is the required  $W/L$  if the circuit must provide a voltage gain of 5 with the value of  $R_D$  obtained in A)?



**Figure 1.**

2. Consider the circuit shown in Figure 2. Find the expression for the small-signal voltage gain. What is the purpose of resistors  $R_1$  and  $R_2$ ?

 

**Figure 2.**

3. Calculate the overall small-signal voltage gain for the configurations shown in Fig. 3. Take a look about How voltage gain changes according to different Mos configurations that look similar at first sight.

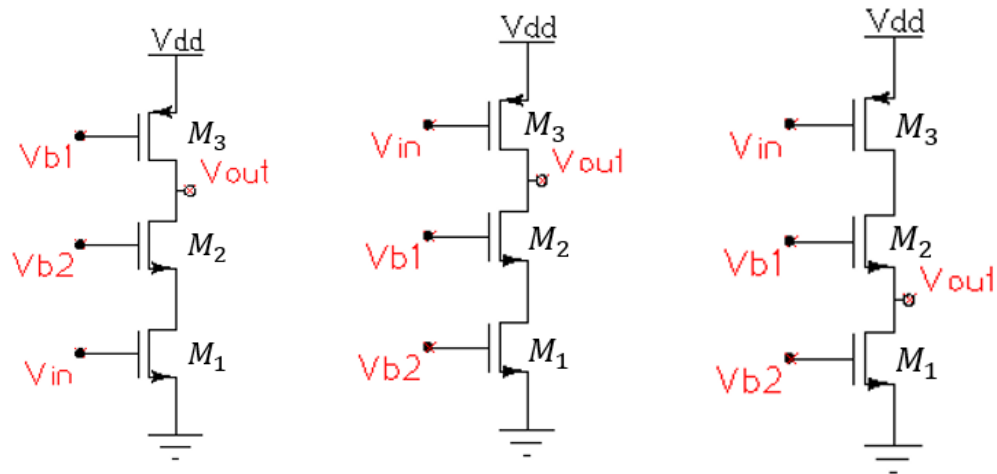


Figure 3.

4. Calculate the small-signal voltage gain of the circuit shown in Figure 4.

 


Figure 4.

5. Assuming all transistors are in saturation, calculate the small-signal voltage gain of the circuit shown in Figure 5.

 


Figure 5.

6. Consider the circuit shown in Figure 6. The purpose is to establish a DC drain current  $I_d = 0.5 \text{ mA}$ . The manufacturer of the transistor specifies  $V_t = 1 \text{ V}$  and  $k_n'W/L = 1 \text{ mA/V}^2$ . Calculate the value of the resistors that meet the requirement. Neglect channel-length modulation and  $V_{dd} = 15 \text{ V}$ .

 


Figure 6.

7. En el circuito siguiente se tiene  $R_1=45k\Omega$ ,  $R_2=5k\Omega$  y  $R_3=45k\Omega$ . Ignore el efecto cuerpo de los transistores que puedan presentar. Para cada transistor calcúlese: **a)** La corriente  $I_D$ , **b)** la transconductancia  $g_m$  y la resistencia  $r_o$  de pequeña señal, **c)** calcule la potencia que consume el circuito.

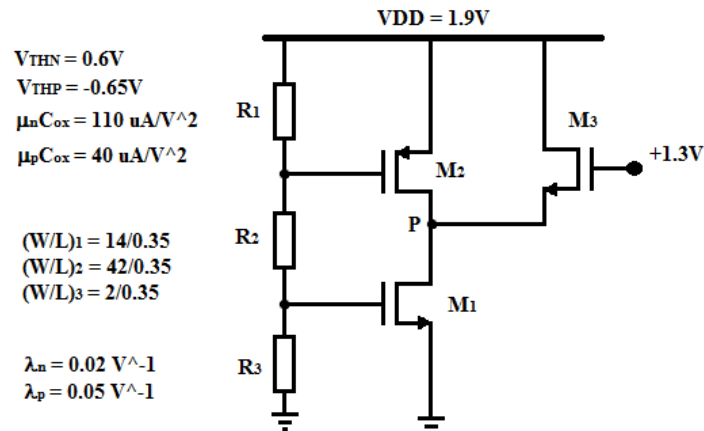


Figure 7.

8. The circuit shown in Figure 8 illustrates a discrete-circuit amplifier. The input signal is coupled to the gate through a very large capacitor as well as the transistor source. The output signal that develops at the drain is coupled to a load resistance via a very large capacitor. Capacitors behave as short circuits for signals and open circuits for DC. Find the voltage gain of the configuration.

 


Figure 8.

9. The circuit shown in Figure 9 produces two outputs. Assume  $\lambda = 0$ . Calculate  $V_{out1}/V_{in}$  and  $V_{out2}/V_{in}$ .

 


Figure 9.

10. Find the output impedance ( $R_{out}$ ) of the configurations illustrated in Fig 10.

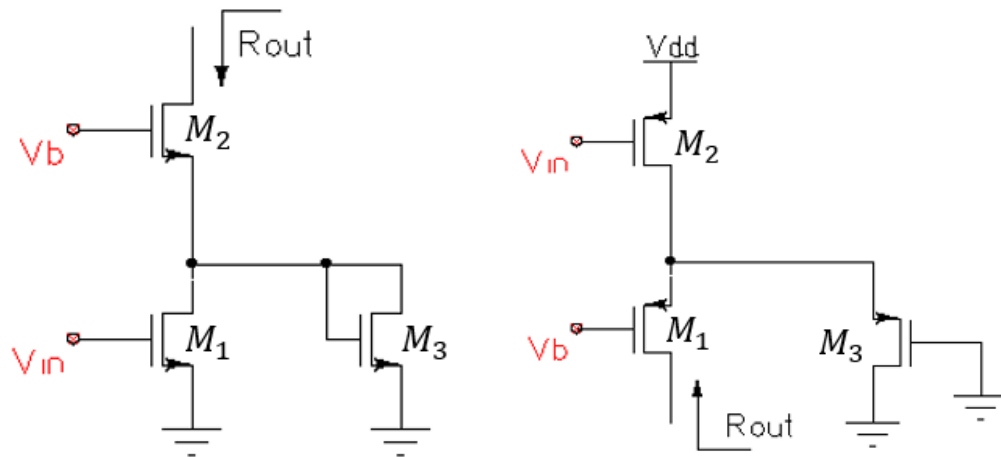


Figure 10.

11. Calculate the small-signal voltage gain of the configurations shown in Fig. 11.

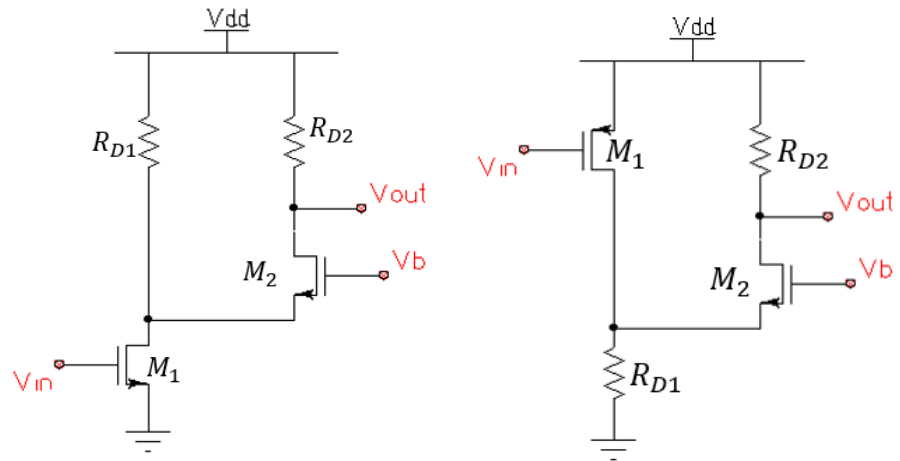


Figure 11.

12. Determine the region of operation (cut-off, triode, saturation) for each of the circuits shown in Figure 12.

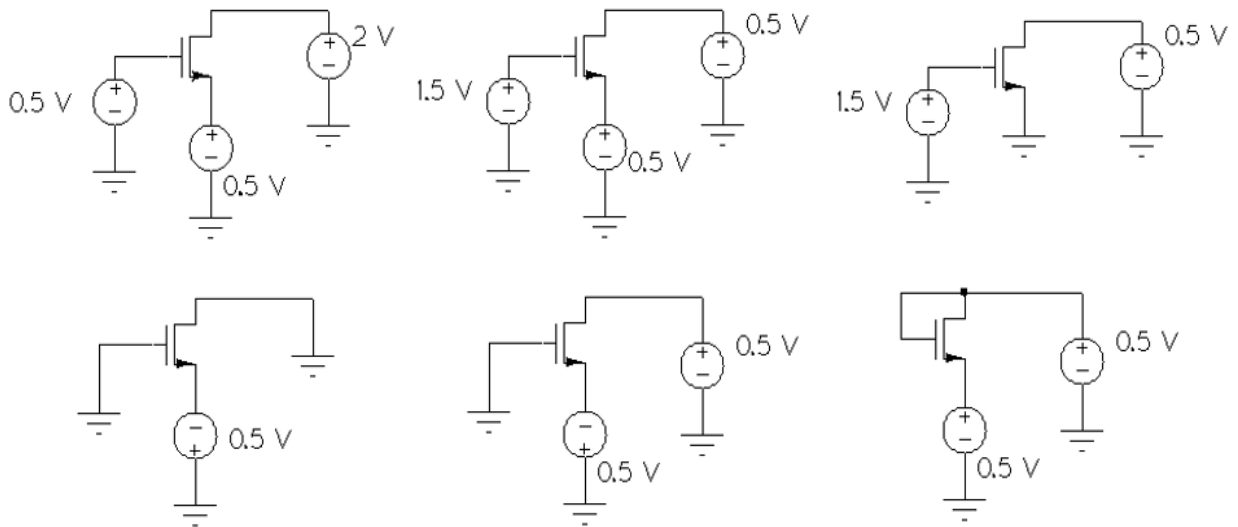


Figure 12.

13. For the circuit shown in Figure 13, plot and clearly label  $i_d$  vs  $v_g$ , with  $V_g$  varying from 0 to 1.8V. The Nmos transistor has  $V_t = 0.4\text{ V}$  and  $k_n'W/L = 1\text{ mA/V}^2$ . Give the equations used for each part of the final graph.

 


Figure 13.

14. Sketch  $I_x$  vs  $V_x$  for the circuit shown in Figure 14.  $V_x$  varies from 0 to 3V. The manufacturer specifies: PMOS Model: Level = 1,  $V_{TO} = -0.8$ ,  $\text{GAMMA} = 0.4$ ,  $U_0 = 100$ ,  $\text{LAMBDA} = 0.2$ ,  $\text{TOX} = 9\text{e-}9$ .

 


Figure 14.

15. Consider the circuit shown in Figure 15. Sketch  $I_x$  vs  $V_x$ .  $V_x$  varies from 0 to  $V_{DD}$ .  $V_{DD} = 3V$ . The manufacturer specifies: PMOS Model: Level = 1,  $V_{TO} = -0.8$ ,  $\text{GAMMA} = 0.4$ ,  $U_0 = 100$ ,  $\text{LAMBDA} = 0.2$ ,  $\text{TOX} = 9e-9$ .

 


Figure 15.