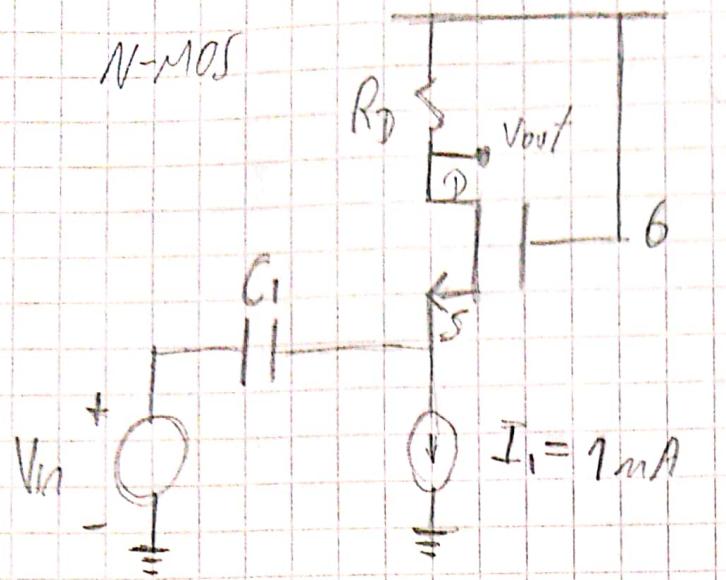


1)

$$V_{DD} = 1,8$$

N-MOS




$$\mu_n C_{ox} = 200 \mu A/V^2$$

$$\mu_p C_{ox} = 100 \mu A/V^2$$

$$\lambda = 0$$

$$V_{TN} = 0,8 \text{ V} \rightarrow \text{N-MOS}$$

$$V_{TH} = -0,4 \text{ V} \rightarrow \text{P-MOS}$$

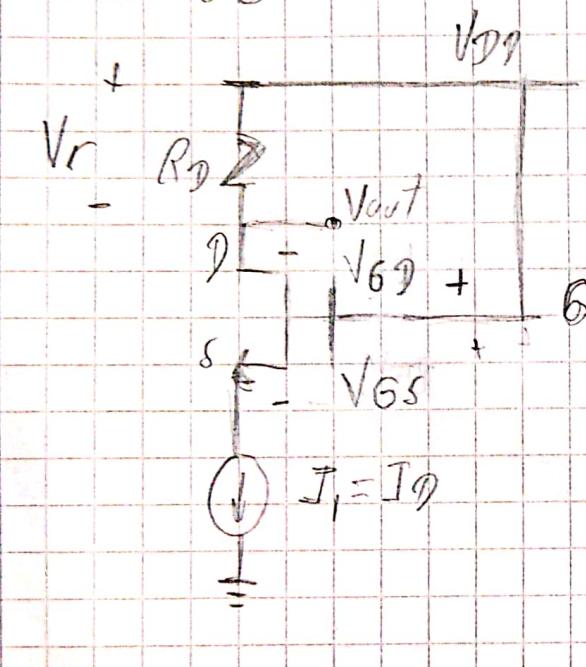A)  $E_1 \quad D_C$ 

$$V_{DS} = V_{GS} - V_{TH} + 0,1$$

$$V_{DS} = 1,8 - 0,4 + 0,1 = 1,5 \text{ V}$$


$$V_{out} = V_{DS} = 1,5 \text{ V}$$

$$R_D = \frac{V_{DD} - V_{out}}{1 \cdot 10^{-3}} =$$

$$= \frac{1,8 - 1,5}{1 \cdot 10^{-3}} = \frac{0,3}{1 \cdot 10^{-3}} = 300 \Omega$$

b)

en AC

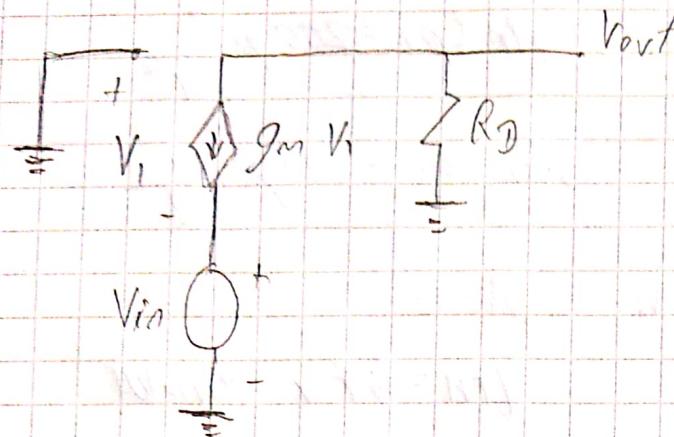

$$V_{out} = -g_m (-V_{in}) R_D$$

$$\frac{V_{out}}{V_{in}} = g_m \cdot R_D$$

$$\sqrt{2N_n C_o x} \frac{V}{L} I_D = \frac{5}{300}$$



$$5 = g_m \cdot 300$$

$$g_m = \frac{5}{300} = 0,016666666666666666$$

$$\left(\frac{5}{300}\right)^2 = 2 N_n C_o x \frac{W}{L} I_D$$

$$\frac{W}{L} = \frac{\left(\frac{5}{300}\right)^2}{2 \cdot 200 \cdot 10^{-6} \cdot 1 \cdot 10^{-3}} = 694,4$$

2

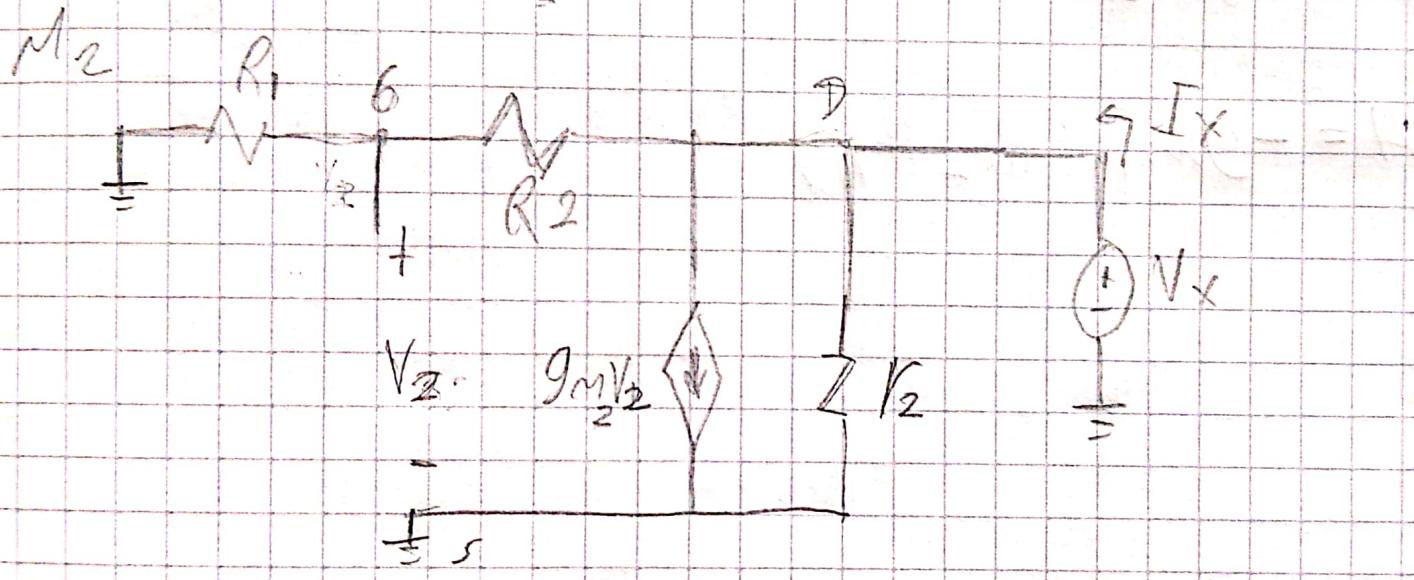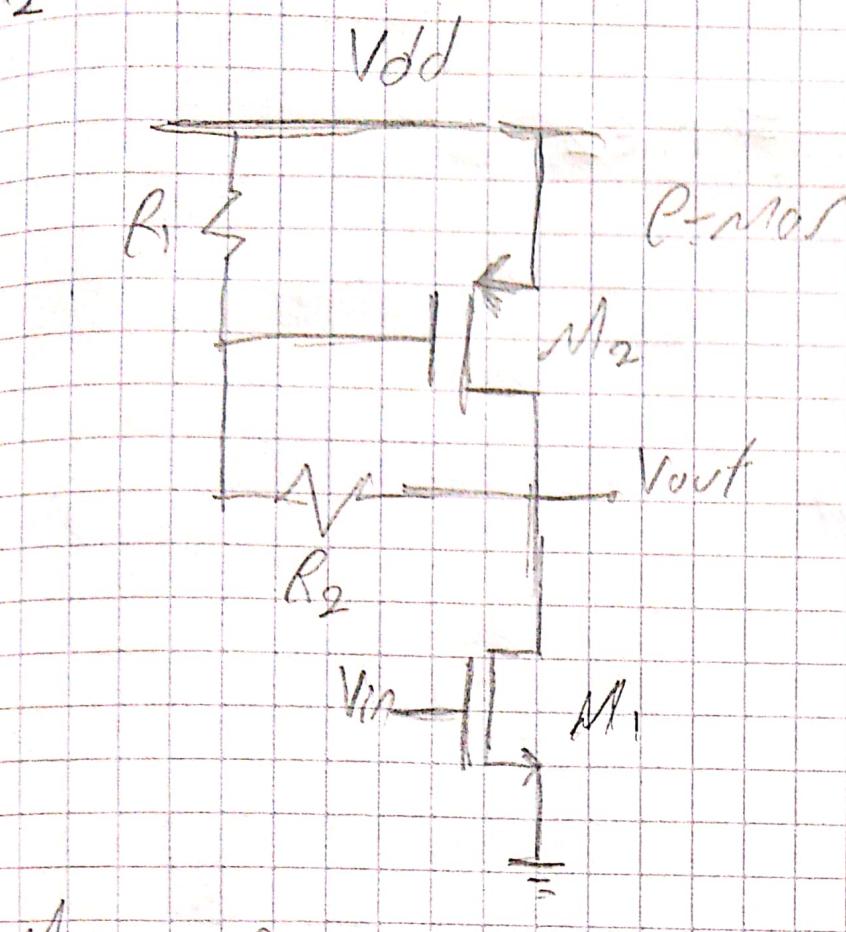


$$V_2 = \frac{V_X R_1}{R_1 + R_2}$$

$$I_X = g_{m2} V_2 + \frac{V_X}{R_2}$$

$$I_X = g_{m2} \frac{V_X R_1}{R_1 + R_2} + \frac{V_X}{R_2} = V_X \left( \frac{(g_{m2} R_1) R_2 + R_1 + R_2}{(R_1 + R_2) R_2} \right)$$

$$\frac{V_x}{I_x} = \frac{(R_1 + R_2) R_2}{(g_m R_1) R_2 + R_1 + R_2} = R_{eq}$$


M.

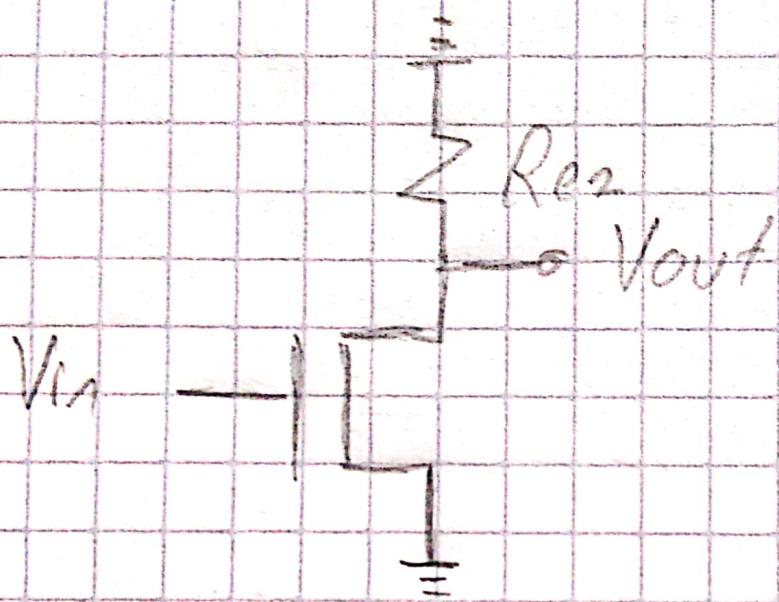

Common Source

$$A = -g_m \left( R_{eq} || k_f \right)$$

3)

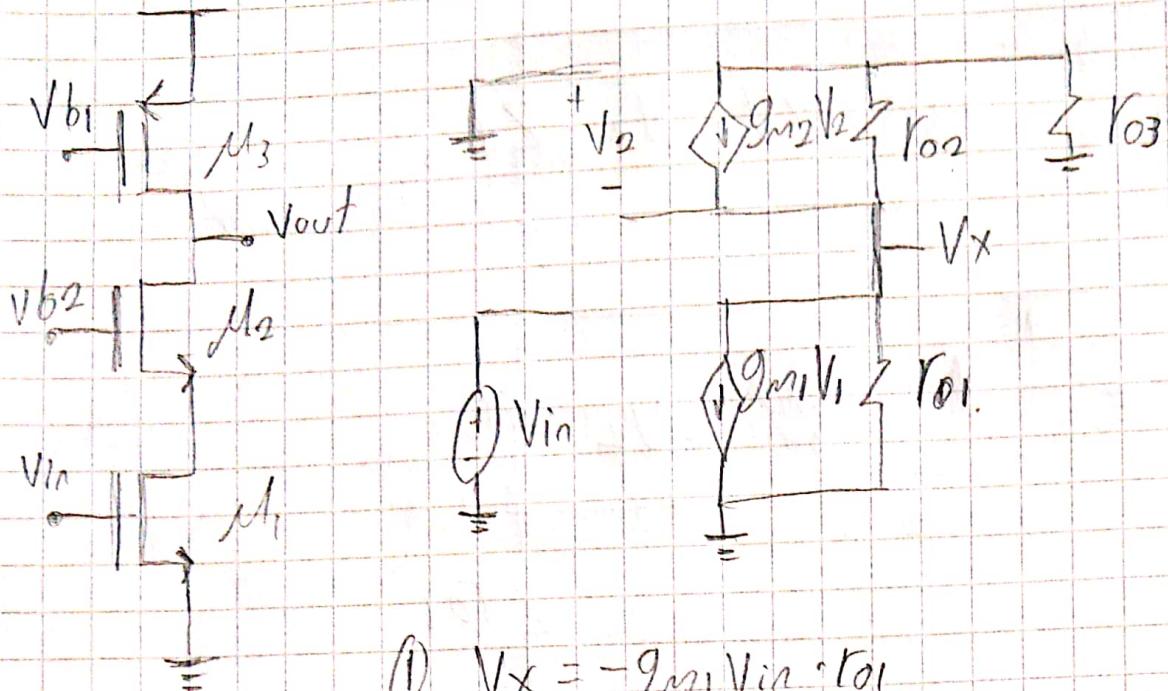

$$\textcircled{1} \quad V_x = -g_{m1} V_{in} \cdot r_{o1}$$

$$g_{m2}(-V_x) + \frac{V_{out} - V_x}{r_{o2}} + \frac{V_{out}}{r_{o3}} = 0$$


$$-V_x \left( g_{m2} + \frac{1}{r_{o2}} \right) + V_{out} \left( \frac{1}{r_{o2}} + \frac{1}{r_{o3}} \right) = 0$$

$$\textcircled{2} \quad V_x = V_{out} \left( \frac{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}{g_{m2} + \frac{1}{r_{o2}}} \right)$$

$$\textcircled{1} = \textcircled{2}$$

$$-g_{m1} V_{in} \cdot r_{o1} = V_{out} \left( \frac{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}{g_{m2} + \frac{1}{r_{o2}}} \right)$$
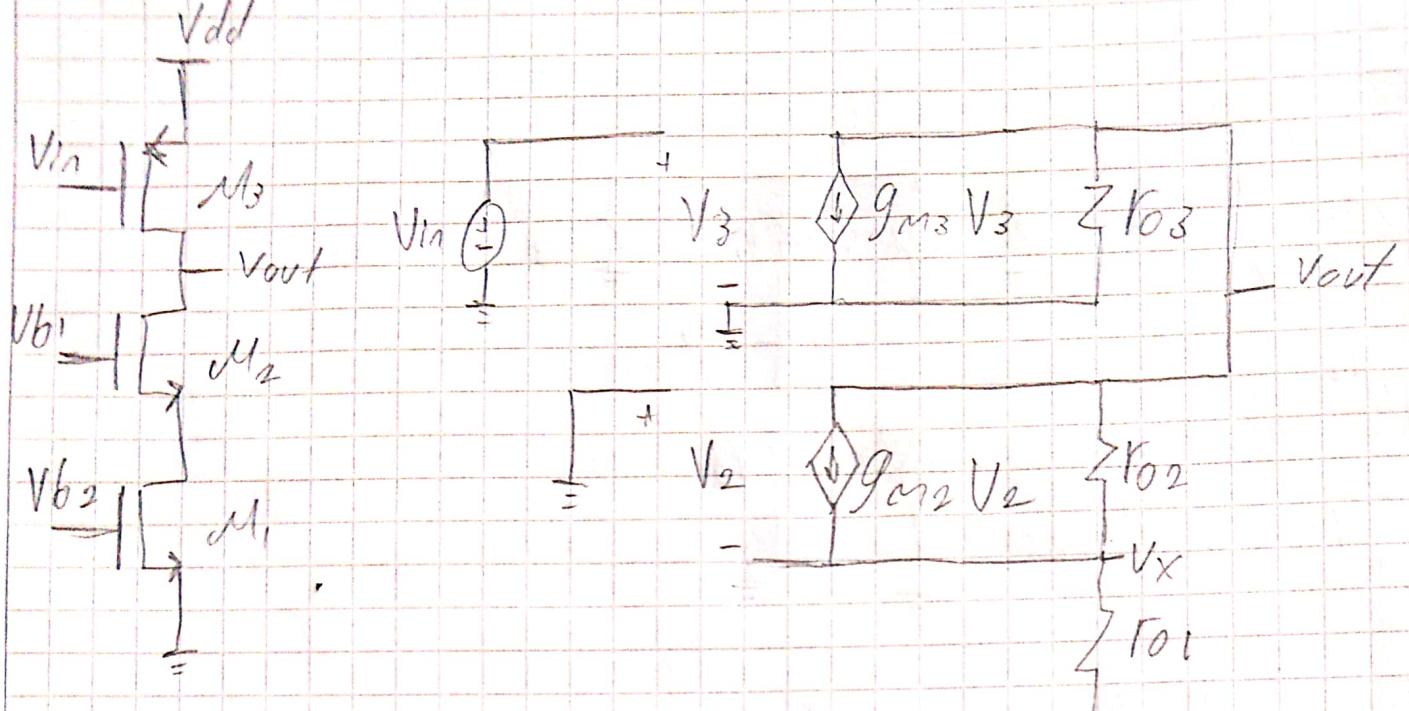
$$\frac{V_{out}}{V_{in}} = \frac{(-g_{m1} \cdot r_{o1})(g_{m2} + \frac{1}{r_{o2}})}{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}$$



$$\frac{V_x}{R_{o1}} = \frac{V_{out} - V_x}{R_{o2}} + g_{m2}(-V_x)$$

$$V_x \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right) = \frac{V_{out}}{R_{o2}}$$

$$\frac{V_x}{V_{out}} = \frac{1}{R_{o2} \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right)} \quad ①$$

$$\frac{V_{out}}{R_{o3}} + g_{m3}V_{in} + \frac{V_{out} - V_x}{R_{o2}} + g_{m2}(-V_x) = 0$$

$$V_{out} \left( \frac{1}{R_{o3}} + \frac{1}{R_{o2}} \right) + g_{m3}V_{in} = V_x \left( g_{m2} + \frac{1}{R_{o2}} \right)$$

$$\frac{1}{R_{o3}} + \frac{1}{R_{o2}} + \frac{g_{m3}V_{in}}{V_{out}} = \frac{V_x}{V_{out}} \left( g_{m2} + \frac{1}{R_{o2}} \right)$$

$$\frac{V_x}{V_{out}} = \frac{\frac{1}{R_{o3}} + \frac{1}{R_{o2}} + \frac{g_{m3}V_{in}}{V_{out}}}{g_{m2} + \frac{1}{R_{o2}}} \quad ②$$

$$\textcircled{1} = \textcircled{2}$$

$$\frac{\frac{1}{r_{03}} + \frac{1}{r_{02}} + \frac{g_{m3} V_{in}}{V_{out}}}{r_{02} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} + g_{m2} \right)} = g_{m2} + \frac{1}{r_{02}}$$


$$\frac{\frac{1}{r_{02}} + g_{m2}}{r_{02} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} + g_{m2} \right)} = \frac{1}{r_{03}} + \frac{0}{r_{02}} + \frac{g_{m3} V_{in}}{V_{out}}$$

$$\frac{\frac{1}{r_{02}} + g_{m2}}{r_{02} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} + g_{m2} \right)} - \frac{1}{r_{03}} - \frac{1}{r_{02}} = \frac{g_{m3} V_{in}}{V_{out}}$$

$$\frac{\frac{1}{r_{02}} + g_{m2}}{r_{02} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} + g_{m2} \right)} - \frac{1}{r_{03}} - \frac{1}{r_{02}} = \frac{V_{in}}{V_{out}}$$

$\cancel{g_{m3}}$
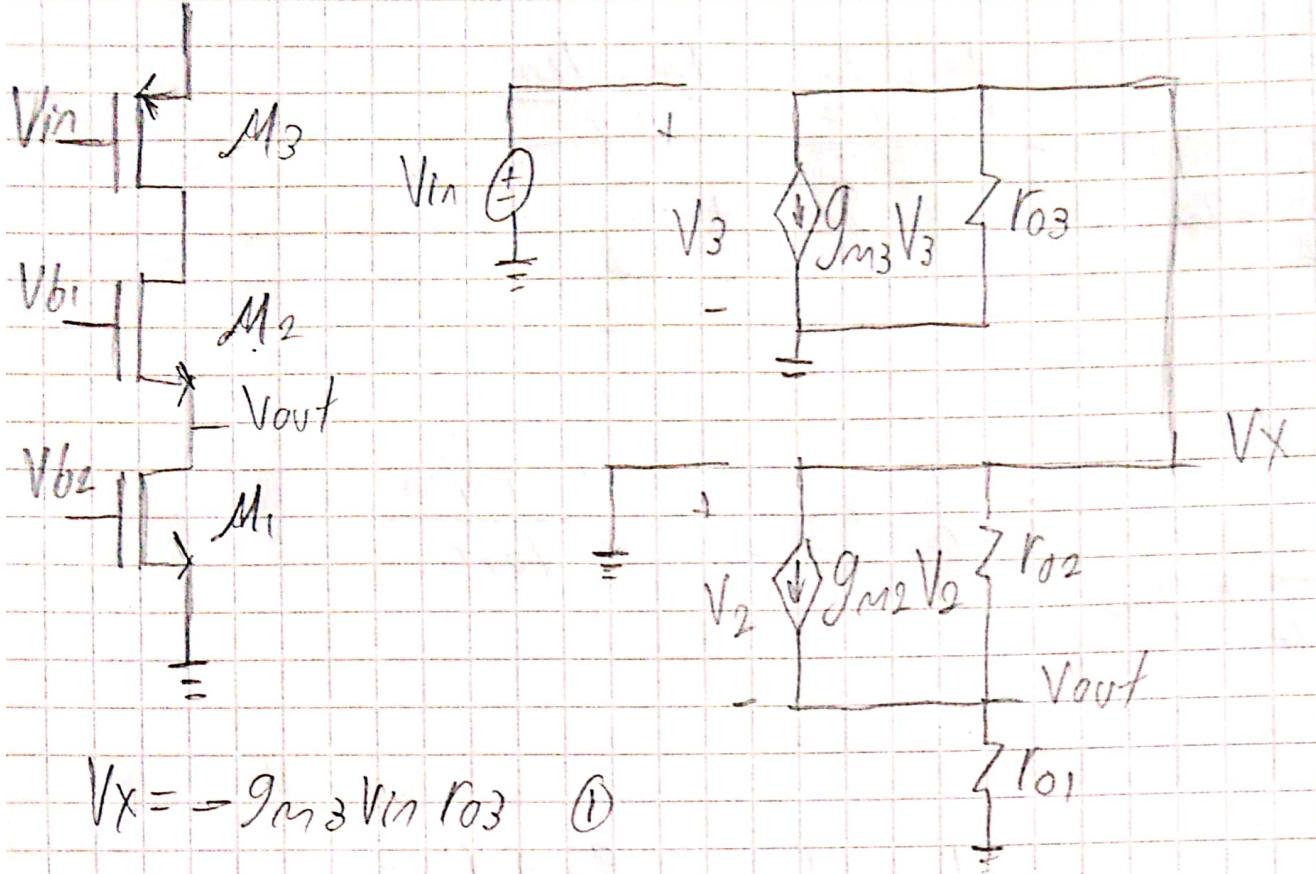
$$\frac{V_{out}}{V_{in}} = \frac{g_{m3}}{\frac{\frac{1}{r_{02}} + g_{m2}}{r_{02} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} + g_{m2} \right)} - \frac{1}{r_{03}} - \frac{1}{r_{02}}}$$



$$\frac{V_x}{R_{o2}} = \frac{V_x - V_{out}}{R_{o2}} + g_{m2}(-V_{out}) \quad (1)$$


$$\frac{V_x}{R_{o2}} = V_{out} \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right)$$

$$V_x = V_{out} R_{o2} \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right) \quad (2)$$

$$(1) = (2)$$

$$g_{m3} V_{in} R_{o3} = V_{out} R_{o2} \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right)$$
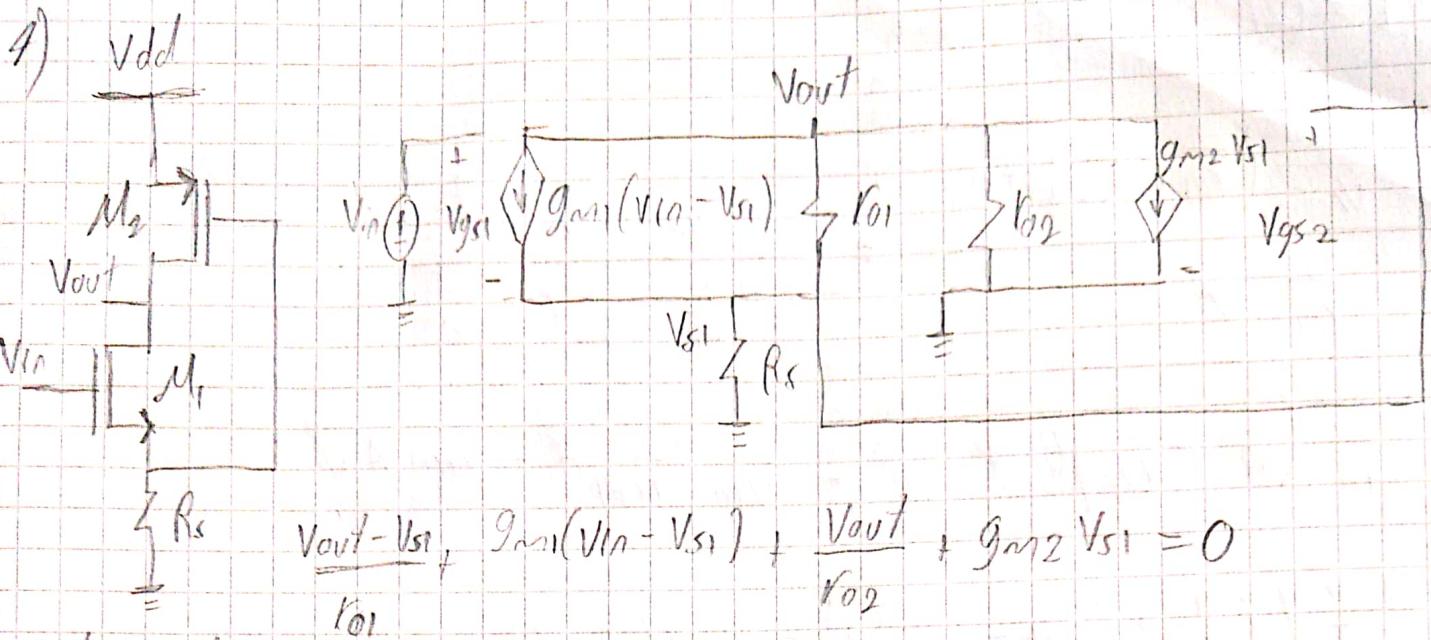
$$\frac{V_{out}}{V_{in}} = \frac{-g_{m3} R_{o3}}{R_{o2} \left( \frac{1}{R_{o1}} + \frac{1}{R_{o2}} + g_{m2} \right)}$$



Node  $V_{out}$

$$V_{s1} \left( \frac{1}{R_{f1}} + g_{m1} - g_{m2} \right) = V_{out} \left( \frac{1}{R_{f1}} + \frac{1}{R_{f2}} \right) + V_{in} g_{m1}$$

$$V_{s1} = \frac{V_{out} \left( \frac{1}{R_{f1}} + \frac{1}{R_{f2}} \right) + V_{in} g_{m1}}{\frac{1}{R_{f1}} + g_{m1} - g_{m2}} \Rightarrow \frac{V_{s1}}{V_{in}} = \frac{\frac{V_{out}}{R_{f1}} + \frac{1}{R_{f2}}}{\frac{1}{R_{f1}} + g_{m1} - g_{m2}} + g_{m1}$$

(1)

Node  $V_{s1}$

$$\frac{V_{s1}}{R_s} = g_{m1}(V_{in} - V_{s1}) + \frac{V_{out} - V_{s1}}{R_{f1}}$$

$$V_{s1} \left( \frac{1}{R_s} + \frac{1}{R_{f1}} + g_{m1} \right) = \frac{V_{out}}{R_{f1}} + g_{m1} V_{in}$$

$$V_{s1} = \frac{\frac{V_{out}}{R_{f1}} + g_{m1} V_{in}}{\frac{1}{R_s} + \frac{1}{R_{f1}} + g_{m1}}$$

$$\frac{V_{s1}}{V_{in}} = \frac{\frac{V_{out}}{R_{f1}} + g_{m1} V_{in}}{\frac{1}{R_s} + \frac{1}{R_{f1}} + g_{m1}} \quad (2)$$

B

$$\textcircled{1} = \textcircled{2}$$


$$\frac{\frac{V_{out}}{V_{in}} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} \right) + g_{m1}}{A} = \frac{\frac{V_{out}}{V_{in}} \left( \frac{1}{r_{01}} \right) + g_{m1}}{B}$$

$$\frac{V_{out}}{V_{in}} \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} \right) B + g_{m1} B = \frac{V_{out}}{V_{in}} \left( \frac{1}{r_{01}} \right) A + g_{m1} A$$

$$\frac{V_{out}}{V_{in}} \left( \left( \frac{1}{r_{01}} + \frac{1}{r_{02}} \right) B - \left( \frac{1}{r_{01}} \right) A \right) = g_{m1} (A - B)$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (A - B)}{\left( \frac{1}{r_{01}} + \frac{1}{r_{02}} \right) B - \left( \frac{1}{r_{01}} \right) A}$$

5)

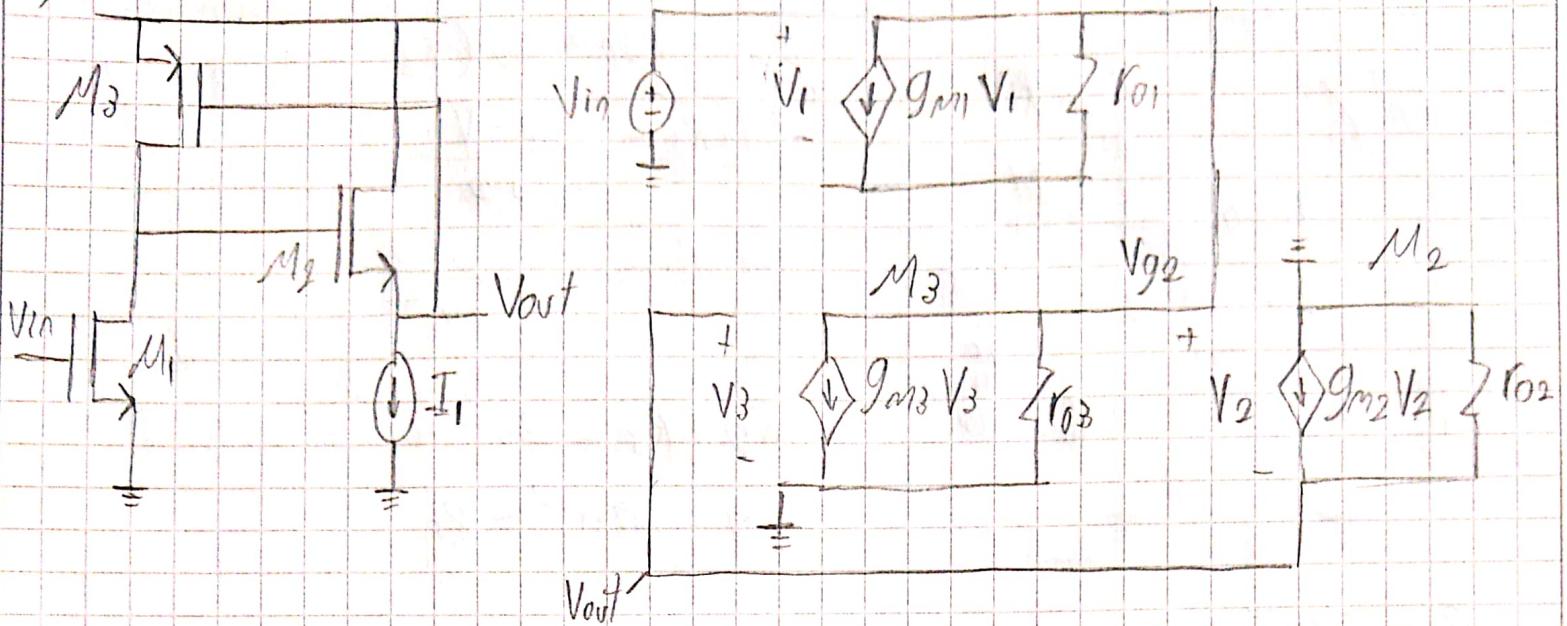V<sub>old</sub>

$$V_3 = V_{out} \quad V_1 = V_{in} \quad V_2 = V_{g2} - V_{out}$$

Para  $V_{g2}$ 

$$\frac{V_{g2}}{R_{o1}} + \frac{V_{g2}}{R_{o3}} + g_{m1} V_{in} + g_{m3} V_{out} = 0 \quad (1)$$

Para  $V_{out}$ 

$$\frac{V_{out}}{R_{o2}} - g_{m2} (V_{g2} - V_{out}) = 0$$

$$V_{g2} = \frac{V_{out}}{g_{m2}} \left( \frac{g_{m2} R_{o2} + 1}{R_{o2}} \right) \quad (2)$$


(2) en (1)

$$\frac{V_{out}}{g_{m2}} \left( \frac{g_{m2} R_{o2} + 1}{R_{o2}} \right) \left( \frac{R_{o3} + R_{o1}}{R_{o1} \cdot R_{o3}} \right) + g_{m1} V_{in} + g_{m3} V_{out} = 0$$

$$V_{out} \left( \underbrace{\left( \frac{1}{g_{m2}} \right) \left( \frac{g_{m2} R_{o2} + 1}{R_{o2}} \right) \left( \frac{R_{o3} + R_{o1}}{R_{o1} \cdot R_{o3}} \right)}_A + g_{m3} \right) = - g_{m1} V_{in}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1}}{A}$$

b)

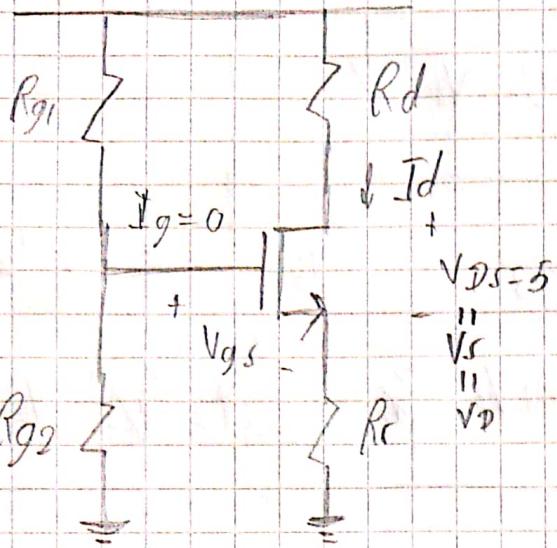

$$V_{DS} - V_{DD} = I_D (R_d + R_s)$$

$$R_d + R_s = \frac{V_{DD} - V_{DS}}{I_D}$$

$$R_d + R_s = \frac{15 - 5}{0,5 \times 10^{-3}}$$

$$R_d + R_s = 20 \cdot 10^3$$

$$R_d = 20 \cdot 10^3 - R_s$$

$$R_s = \frac{V_{DS}}{I_D} = \frac{5}{0,5 \cdot 10^{-3}} = 10 \cdot 10^3 = 10 \text{ k}\Omega$$

$$R_d = 20 \cdot 10^3 - 10 \cdot 10^3 = 10 \text{ k}\Omega$$

N-MOS en saturación

$$I_D = \frac{1}{2} M_n C_{OX} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$0,5 \cdot 10^{-3} = \frac{1}{2} \cdot 1 \cdot 10^{-3} (V_{GS} - V_{TH})^2$$

$$0,5 \cdot 10^{-3} = 0,5 \cdot 10^{-3} (V_{GS} - V_{TH})^2$$

$$\sqrt{I} = (V_{GS} - V_{TH})$$

$$I = V_{GS} - V_{TH}$$

$$I = V_{GS} - 1$$

$$V_{GS} = 2$$

$$V_{GS} = V_6 - V_S$$

$$V_6 = V_{GS} + V_S$$

$$V_6 = 2 + 5$$

$$V_6 = 7 \text{ V}$$



$$R_{61} = \frac{V_{DD}}{V_6} R_{ST}$$

$$R_{62} = \frac{V_{DD}}{V_{DD} - V_6} R_{ST}$$

$$R_{61} = 8 \text{ M}\Omega$$

$$R_{62} = 7 \text{ M}\Omega$$



8)

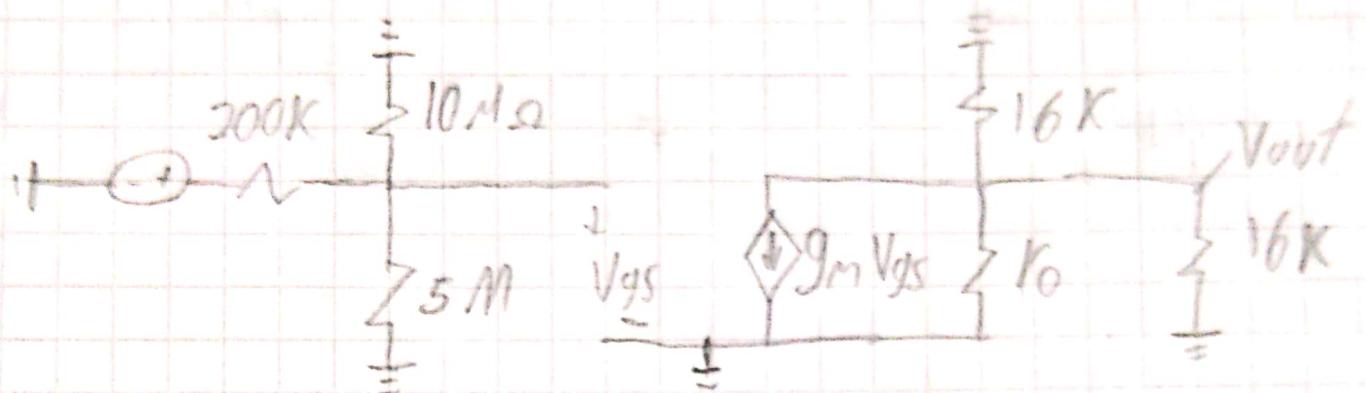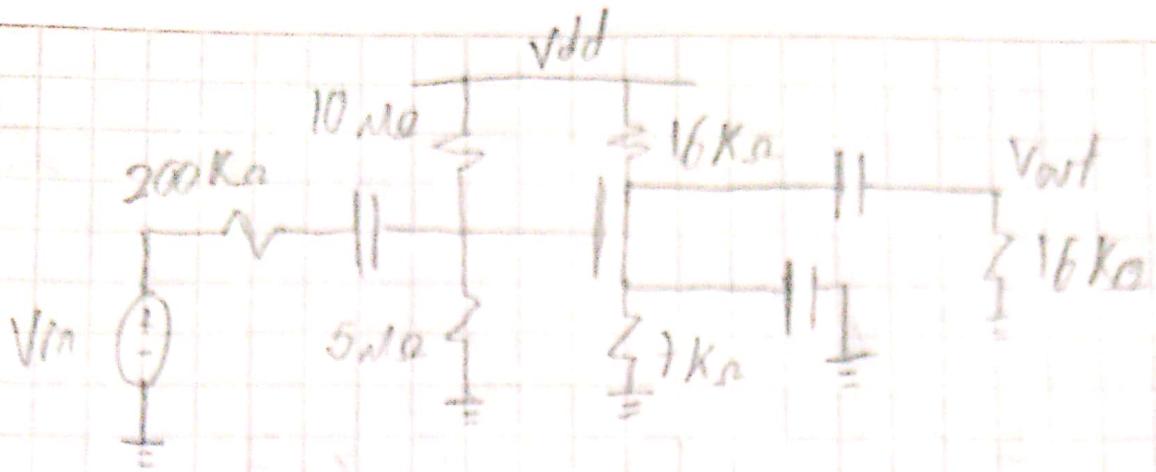

$$V_{gs} = \frac{V_{in} (10M \parallel 5M)}{200K + (10M \parallel 5M)} = V_{in} \frac{50}{53}$$

$$V_{out} = -g_m \left( V_{in} \frac{50}{53} \right) \cdot (r_o \parallel 16K \parallel 16K)$$
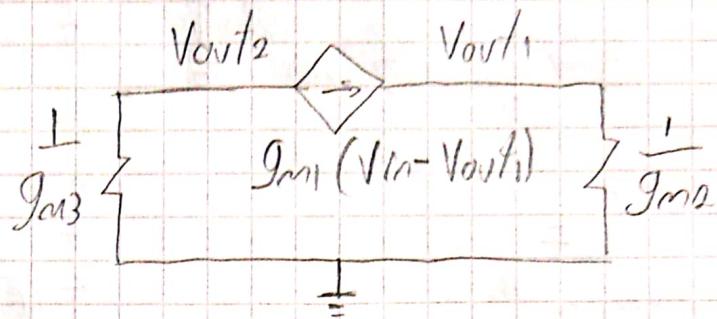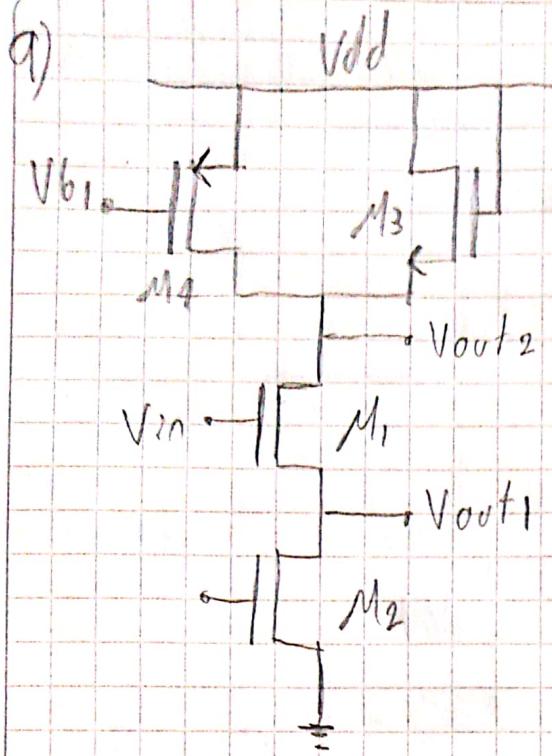
$$\frac{V_{out}}{V_{in}} = -g_m \left( \frac{50}{53} \right) \cdot (r_o \parallel 16K \parallel 16K)$$



$$\frac{V_{out1}}{\frac{1}{g_m2}} = g_{m1}(V_{in} - V_{out1})$$

$$\frac{V_{out2}}{\frac{1}{g_m3}} = g_{m1}(V_{in} - V_{out1})$$

$$V_{out1} g_{m2} = g_{m1} V_{in} - g_{m1} V_{out1}$$

$$V_{out2} g_{m3} = -g_{m1} V_{in} + V_{out1} g_{m1}$$

$$V_{out1} (g_{m2} + g_{m1}) = g_{m1} V_{in}$$

$$V_{out1} = \frac{V_{out2} g_{m3} + V_{in} g_{m1}}{g_{m1}}$$

$$V_{out1} = \frac{g_{m1} V_{in}}{g_{m1} + g_{m2}} \quad (1)$$

$$V_{out1} = \frac{V_{out2} g_{m3}}{g_{m1}} + V_{in} \quad (2)$$

$$\frac{V_{out1}}{V_{in}} = \frac{g_{m1}}{g_{m1} + g_{m2}} //$$

$$(1) = (2)$$

$$\frac{g_{m1} V_{in}}{g_{m2} + g_{m1}} = \frac{V_{out2} g_{m3}}{g_{m1}} + V_{in}$$

$$\frac{V_{out2} g_{m3}}{g_{m1}} = \frac{g_{m1} V_{in}}{g_{m2} + g_{m1}} - V_{in}$$




$$\frac{V_{out2} g_{m3}}{g_{m1}} = V_{in} \left( \frac{g_{m1}}{g_{m2} + g_{m1}} - 1 \right)$$

$$\frac{V_{out2} g_{m3}}{g_{m1}} = V_{in} \left( \frac{g_{m1} - g_{m2} - g_{m1}}{g_{m2} + g_{m1}} \right)$$

$$\frac{V_{out2} g_{m2}}{g_{m1}} = V_{in} \left( \frac{-g_{m2}}{g_{m2} + g_{m1}} \right)$$

$$\frac{V_{out2}}{V_{in}} = \frac{-g_{m2} g_{m1}}{g_{m2} g_{m3} + g_{m1} g_{m3}}$$

10)

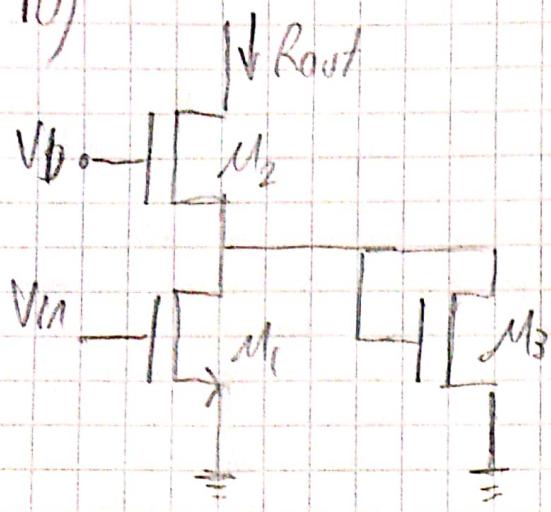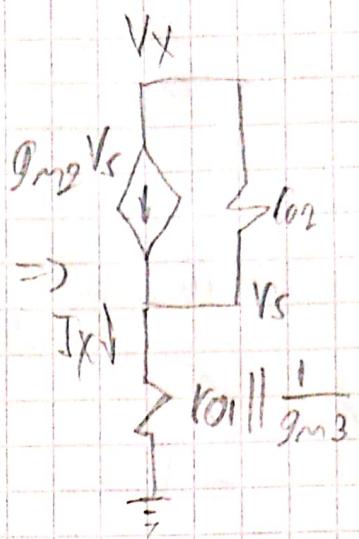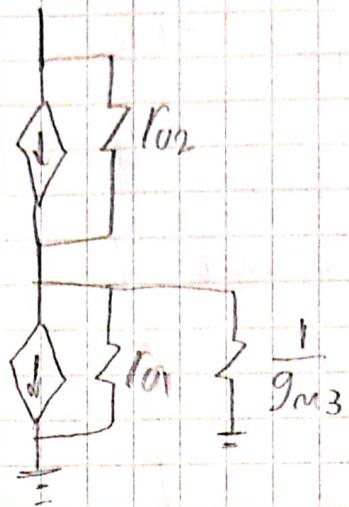 $\Rightarrow$ 

$$I_x = \frac{V_s}{R_o \parallel \frac{1}{g_m3}} = g_m2(-V_s) + \frac{V_x - V_s}{R_o2} \quad ①$$


$$V_s = I_x \left( R_o1 \parallel \frac{1}{g_m3} \right) \quad ②$$

① on ②

$$I_x = -g_m2 \left( I_x \left( R_o1 \parallel \frac{1}{g_m3} \right) \right) + \frac{V_x - (I_x (R_o1 \parallel \frac{1}{g_m3}))}{R_o2}$$

$$I_x \left( 1 + g_m2 (R_o1 \parallel \frac{1}{g_m3}) + \frac{R_o1 \parallel \frac{1}{g_m3}}{R_o2} \right) = \frac{V_x}{R_o2}$$
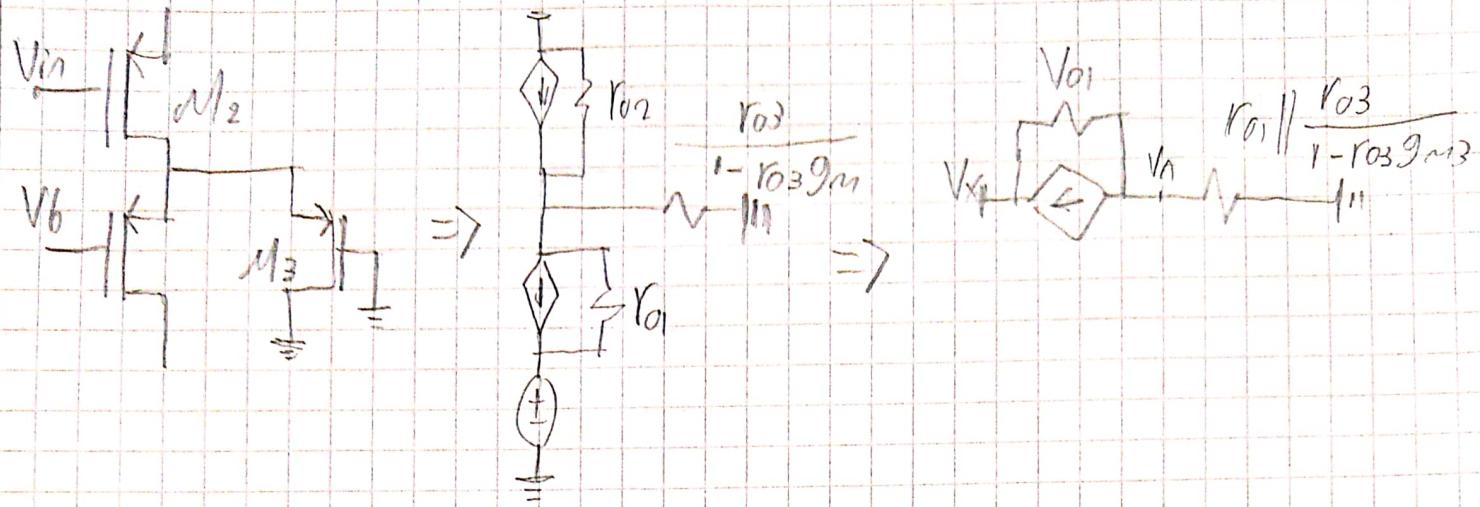
$$\frac{V_x}{I_x} = R_o2 + g_m2 R_o2 \left( R_o1 \parallel \frac{1}{g_m3} \right) + R_o \parallel \frac{1}{g_m3}$$



$$I_x = \frac{V_A}{R_{02} \parallel \frac{R_{02}}{1 - R_{03}g_m}} = I_x \left( R_{02} \parallel \frac{R_{03}}{1 - R_{02}g_m} \right)$$

$$I_x = \frac{V_A - V_A}{R_{02}} - g_m V_A$$

$$I_x \left( 1 + \frac{R_{02} \parallel \frac{R_{03}}{1 - R_{02}g_m}}{R_{01}} + g_m \left( R_{02} \parallel \frac{R_{03}}{1 - R_{02}g_m} \right) \right)$$

$$\frac{V_x}{I_x} = R_{01} + \frac{R_{02} \parallel \frac{R_{03}}{1 - R_{03}g_m}}{R_{03}} + \frac{g_m R_{02} \parallel \frac{R_{03}}{1 - R_{02}g_m}}{R_{01}}$$

(12)

Orden del ejercicio

①      ②      ③

④      ⑤      ⑥

1) OFF  $\rightarrow V_{DS} = 0$

2) Triodo  $\rightarrow V_{DS} > V_{TH}$      $V_{DS} \ll 2(V_{DS} - V_{TH})$

3) Triodo  $\rightarrow V_{DS} > V_{TH}$      $V_{DS} < (V_{DS} - V_{TH})$

4) saturacion  $\rightarrow V_{DS} > V_{TH}$      $V_{DS} > (V_{DS} - V_{TH})$

5) saturacion  $\rightarrow V_{DS} > V_{TH}$      $V_{DS} > (V_{DS} - V_{TH})$

6) OFF  $\rightarrow V_{DS} = 0$